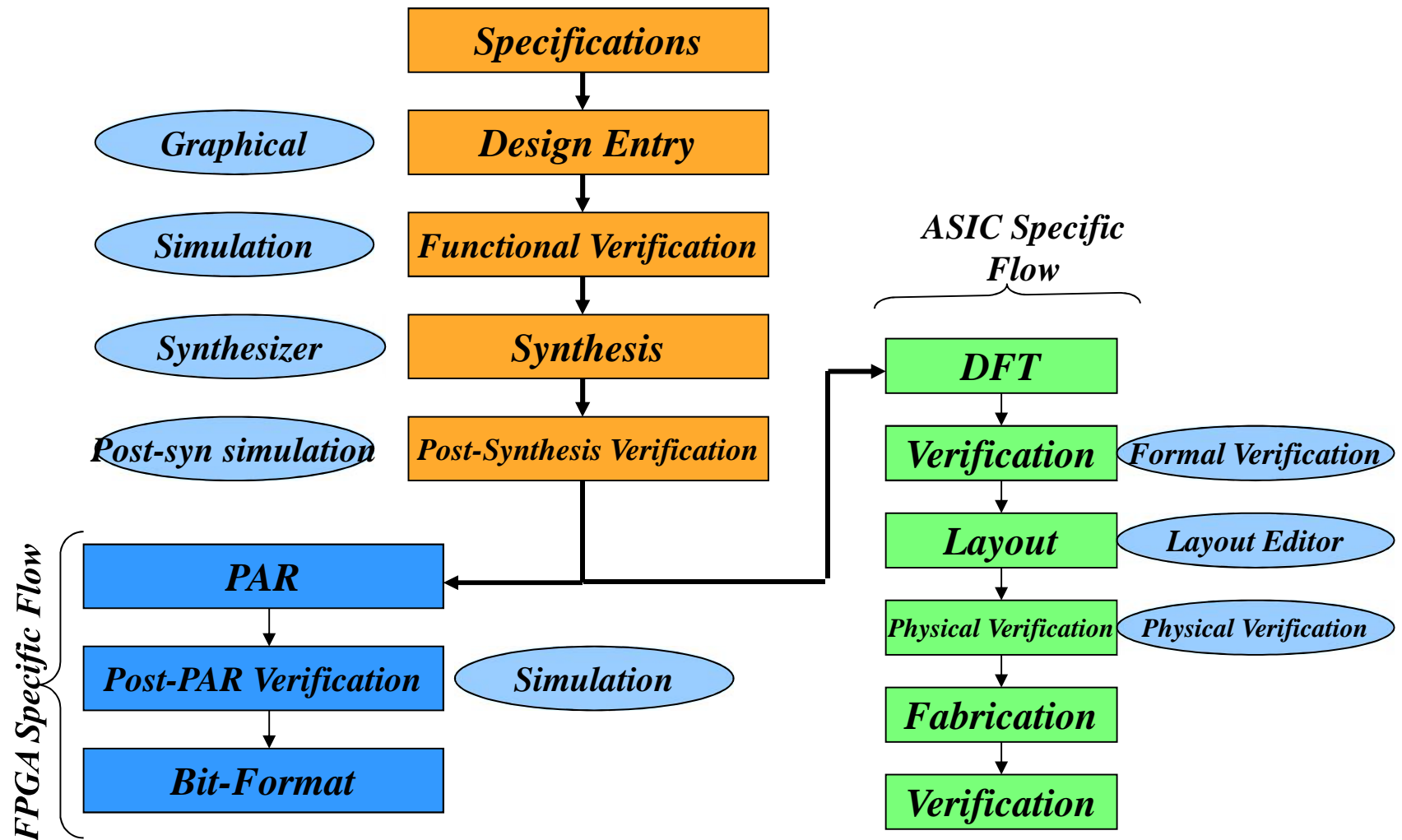


# DIGITAL SYSTEM DESIGN USING VERILOG

# CONTENTS

- Introduction : Need for Hardware Description Languages
- Modeling of combinational logic circuits
- Modeling of sequential logic circuits
- Simple Test Bench & Functional Simulation
- Design entry methods
- Functional Simulation
- Concepts of Logic Synthesis & Synthesis guidelines

# DESIGN FLOW IN ASIC / FPGA



# NEED FOR HARDWARE DESCRIPTION LANGUAGE (HDL)

## **Model, Represent, And Simulate Digital Hardware**

- Hardware Concurrency
- Parallel Activity Flow
- Semantics for Signal Value And Time

## **Special Constructs And Semantics**

- Edge Transitions
- Propagation Delays
- Timing Checks

# VERILOG HDL

## **Basic Unit – A module**

### **Module**

- Describes the functionality of the design
- States the input and output ports

### **Example: A Computer**

- Functionality: Perform user defined computations
- I/O Ports: Keyboard, Mouse, Monitor, Printer

# MODULE

## General definition

```
module module_name ( port_list );  
    port declarations;  
    ...  
    variable declaration;  
    ...  
    description of behavior  
endmodule
```

## Example

```
module HalfAdder (A, B, Sum Carry);  
    input A, B;  
    output Sum, Carry;  
    assign Sum = A ^ B;  
    //^ denotes XOR  
    assign Carry = A & B;  
    // & denotes AND  
endmodule
```

# CONVENTIONS

## Comments

// Single line comment

/\* Another single line comment \*/

/\* Begins multi-line (block) comment

    All text within is ignored

    Line below ends multi-line comment

\*/

## Number

decimal, hex, octal, binary

unsized decimal form

size base form

include underlines, +,-

## String

" Enclose between quotes on a single line"

# CONVENTIONS (CONT.)

## Identifier

A ... Z

a ... z

0 ... 9

Underscore

**Strings are limited to 1024 chars**

**First char of identifier must not be a digit**

**Keywords**

**Operators**

**Verilog is case sensitive**




# DESCRIPTION STYLES

**Structural:** Logic is described in terms of Verilog gate primitives

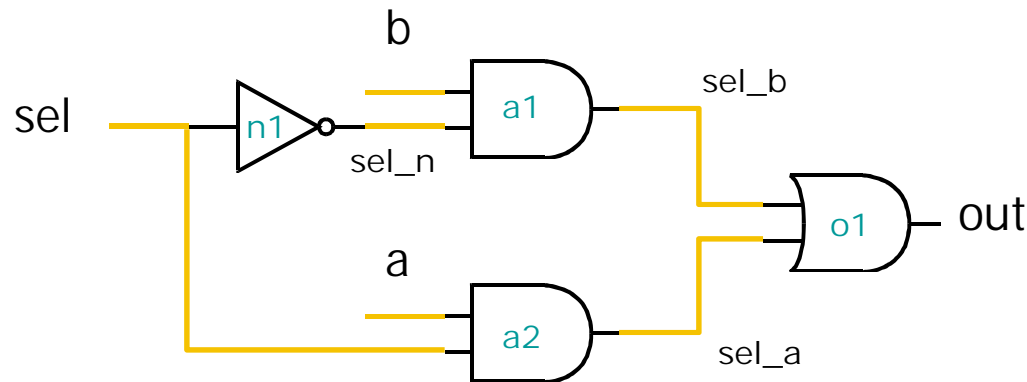**Example:**

```
not n1(sel_n, sel);  
and a1(sel_b, b, sel_b);  
and a2(sel_a, a, sel);  
or o1(out, sel_b, sel_a);
```




# DESCRIPTION STYLES

**Dataflow: Specify output signals in terms of input signals**

**Example:**

**assign** out = (sel & a) | (~sel & b);

 


# DESCRIPTION STYLES

**Behavioral:** Algorithmically specify the behavior of the design

 **Example:**

```
if (select == 0) begin
    out = b;
end
else if (select == 1) begin
    out = a;
end
```



# STRUCTURAL MODELING

**Execution: Concurrent**

**Format (Primitive Gates):**

**and** G2(Carry,A, B);

**First parameter (Carry) – Output**

**Other Inputs (A, B) - Inputs**

# DATAFLOW MODELING

## Uses continuous assignment statement

- Format: **assign** [ delay ] net = expression;
- Example: **assign** sum = a ^ b;

**Delay:** Time duration between assignment from RHS to LHS

**All continuous assignment statements execute concurrently**

**Order of the statement does not impact the design**

# DATAFLOW MODELING

## Delay can be introduced

- Example: `assign #2 sum = a ^ b;`
- “#2” indicates 2 time-units
- No delay specified : 0 (default)

## Associate time-unit with physical time

- ``timescale` time-unit/time-precision
- Example: ``timescale 1ns/100 ps`

## Timescale


``timescale 1ns/100ps`

- 1 Time unit = 1 ns
- Time precision is 100ps (0.1 ns)
- 10.512ns is interpreted as 10.5ns

# DATAFLOW MODELING
 
## Example:

```
`timescale 1ns/100ps
module HalfAdder (A, B, Sum, Carry);
    input A, B;
    output Sum, Carry;
    assign #3 Sum = A ^ B;
    assign #6 Carry = A & B;
endmodule
```






# BEHAVIORAL MODELING

## Example:

```
module mux_2x1 (a, b, sel, out);  
    input a, a, sel;  
    output out;  
    always @(a or b or sel)  
    begin  
        if (sel == 1)  
            out = a;  
        else out = b;  
    end  
endmodule
```



Sensitivity List

# BEHAVIORAL MODELING (CONT.)

## **always** statement : Sequential Block

**Sequential Block: All statements within the block are executed sequentially**

### **When is it executed?**

- Occurrence of an event in the sensitivity list
- Event: Change in the logical value

## **Statements with a Sequential Block: Procedural Assignments**

### **Delay in Procedural Assignments**

- Inter-Statement Delay
- Intra-Statement Delay

# BEHAVIORAL MODELING (CONT.)

## Inter-Assignment Delay

- Example:

Sum = A ^ B;

#2 Carry = A & B;

- Delayed execution

## Intra-Assignment Delay

- Example:

Sum = A ^ B;

Carry = #2 A & B;

- Delayed assignment

# PROCEDURAL CONSTRUCTS

## Two Procedural Constructs

- **initial** Statement
- **always** Statement

**initial** Statement : Executes only once

**always** Statement : Executes in a loop

**Example:**

```
...  
initial begin  
    Sum = 0;  
    Carry = 0;  
end  
...
```

```
...  
always @(A or B) begin  
    Sum = A ^ B;  
    Carry = A & B;  
end  
...
```

# EVENT CONTROL

## Event Control

- Edge Triggered Event Control
- Level Triggered Event Control

## Edge Triggered Event Control

@ (posedge CLK) //Positive Edge of CLK

Curr\_State = Next\_state;

@ negedge	@ posedge
1 → x	0 → x
1 → z	0 → z
1 → 0	0 → 1
x → 0	x → 1
z → 0	z → 1

## Level Triggered Event Control

@ (A or B) //change in values of A or B

Out = A & B;

# LOOP STATEMENTS

## Loop Statements

- Repeat
- While
- For

## Repeat Loop

- Example:  
    repeat (Count)  
        sum = sum + 5;
- If condition is a **x** or **z** it is treated as 0

# LOOP STATEMENTS

## While Loop

- Example:  
    while (Count < 10) begin  
        sum = sum + 5;  
        Count = Count + 1;  
    end
- If condition is a **x** or **z** it is treated as 0

## For Loop

- Example:  
    for (Count = 0; Count < 10; Count = Count + 1) begin  
        sum = sum + 5;  
    end

# CONDITIONAL STATEMENTS

## if Statement

### Format:

```
if (condition)
    procedural_statement
else if (condition)
    procedural_statement
else procedural_statement
```

### Example:

```
if (Clk)
    Q = 0;
else
    Q = D;
```



# CONDITIONAL STATEMENTS

## Case Statement

### Example 1:

```
case (X)
  2'b00: Y = A + B;
  2'b01: Y = A - B;
  2'b10: Y = A / B;
endcase
```

### Example 2:

```
case (3'b101 << 2)
  3'b100: A = B + C;
  4'b0100: A = B - C;
  5'b10100: A = B / C; //This statement is executed
endcase
```

# CONDITIONAL STATEMENTS (CONT.)

## Variants of **case** Statements:

- **casex** and **casez**

**casez** – z is considered as a don't care

**casex** – both x and z are considered as don't cares

## Example:

**casez** (X)

2'b1z: A = B + C;

2'b11: A = B / C;

**endcase**

# DATA TYPES

**Net Types: Physical Connection between structural elements**

**Register Type: Represents an abstract storage element.**

## **Default Values**

- Net Types : z
- Register Type : x

**Net Types: wire, tri, wor, trior, wand, triand, supply0, supply1**

**Register Types : reg, integer, time, real, realtime**

# DATA TYPES

## Net Type: Wire

**wire** [ msb : lsb ] wire1, wire2, ...

- Example

**wire** Reset; // A 1-bit wire

**wire** [6:0] Clear; // A 7-bit wire

## Register Type: Reg

**reg** [ msb : lsb ] reg1, reg2, ...

- Example

**reg** [ 3: 0 ] cla; // A 4-bit register

**reg** cla; // A 1-bit register

# RESTRICTIONS ON DATA TYPES

## Data Flow and Structural Modeling

- Can use only **wire** data type
- Cannot use **reg** data type

## Behavioral Modeling

- Can use only **reg** data type (within initial and always constructs)
- Cannot use **wire** data type

# MODELING OF COMBINATIONAL LOGIC CIRCUITS

```
module ha(a,b,sum,carry);  
    input a,b;  
    output sum,carry;  
    assign sum = a ^ b;  
    assign carry = (a & b);  
endmodule
```

# MODELING OF SEQUENTIAL LOGIC CIRCUITS

```
module counter(  
    input rst,clk,dir,  
    output reg [3:0] q  
);  
always@(posedge (clk))  
begin  
    if (rst)  
        q<=4'b0000;  
    else if (dir)  
        q<=q+4'b0001;  
    else  
        q<=q-4'b0001;  
    end  
endmodule
```

## TEST BENCH AND FUNCTIONAL SIMULATION

```
module counter_test ;  
    wire [3:0] q ;  
    reg  rst ;  
    reg  clk ;  
    reg  dir ;  
    counter  
    DUT (  
        .q (q) ,  
        .rst (rst) ,  
        .clk (clk) ,  
        .dir (dir) );  
  
    // "Clock Pattern" : dutyCycle = 50  
    // Start Time = 0 ns, End Time = 1 us,  
    Period = 20 ns  
    initial  
    begin  
        clk = 1'b0 ;  
        # 10 ;  
        // 10 ns, single loop till start period.  
        repeat(49)  
        begin  
            clk = 1'b1 ;  
            #10 clk = 1'b0 ;  
            #10 ;  
            // 990 ns, repeat pattern in loop.  
        end  
        clk = 1'b1 ;  
        # 10 ;  
        // dumped values till 1 us  
    end  
end
```



# TEST BENCH AND FUNCTIONAL SIMULATION

```
// "Constant Pattern"
```

```
// Start Time = 0 ns, End Time = 1  
us, Period = 0 ns
```

```
initial
```

```
begin
```

```
    rst = 1'b0 ;
```

```
    # 0    rst = 1'b1 ;
```

```
    # 20   rst = 1'b0 ;
```

```
    # 980 ;
```

```
// dumped values till 1 us
```

```
end
```

```
// "Constant Pattern"
```

```
// Start Time = 0 ns, End Time = 1  
us, Period = 0 ns
```

```
initial
```

```
begin
```

```
    dir = 1'b0 ;
```

```
    # 0    dir = 1'b1 ;
```

```
    # 500  dir = 1'b0 ;
```

```
    # 500 ;
```

```
// dumped values till 1 us
```

```
end
```


```
initial
```

```
    #2000 $stop;
```

```
endmodule
```
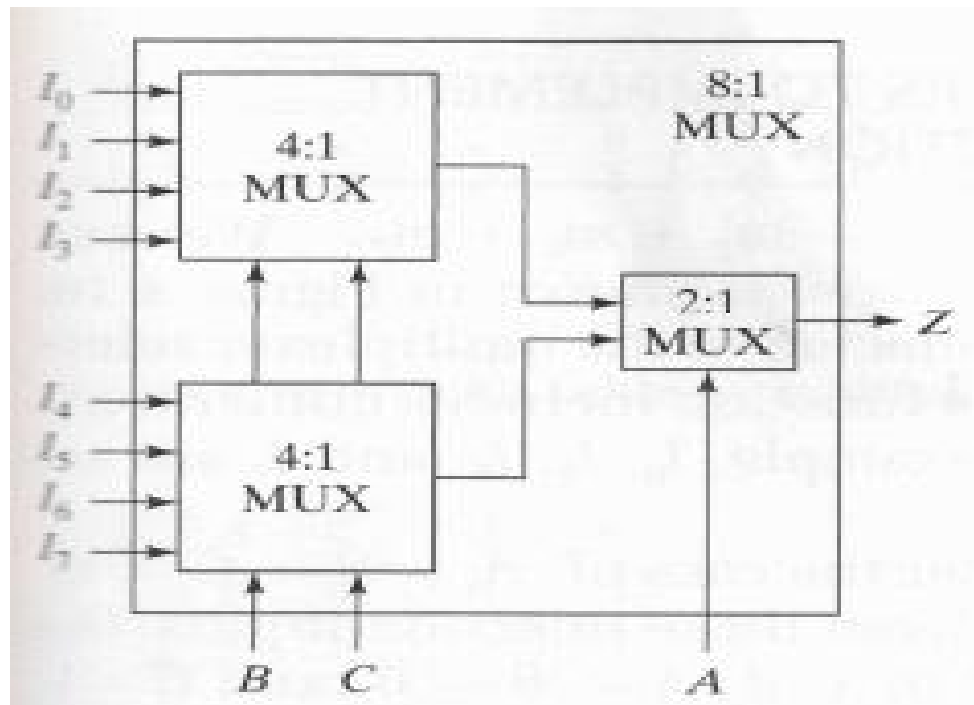
# Exercise

Design a Mux 8:1 using Verilog according to the following structure and verify the functionality using suitable test bench



# EXERCISE

**Write an RTL and Test bench to verify**

- D-flip flop with asynchronous active low reset
- D-flip flop with synchronous active high reset

# MEMORIES

## An array of registers

```
reg [ msb : lsb ] memory1 [ upper : lower ];
```

## Example

```
reg [ 0 : 3 ] mem [ 0 : 63 ];  
// An array of 64 4-bit registers  
reg mem [ 0 : 4 ];  
// An array of 5 1-bit registers
```

# COMPILER DIRECTIVES

**'define** – (Similar to #define in C) used to define global parameter

**Example:**

```
'define BUS_WIDTH 16  
reg [ 'BUS_WIDTH - 1 : 0 ] System_Bus;
```

**'undef** – Removes the previously defined directive

**Example:**

```
'define BUS_WIDTH 16  
...  
reg [ 'BUS_WIDTH - 1 : 0 ] System_Bus;  
...  
'undef BUS_WIDTH
```

# COMPILER DIRECTIVES (CONT.)

**'include** – used to include another file

## **Example**

```
'include "./fulladder.v"
```

# SYSTEM TASKS

## Display tasks

- `$display` : Displays the entire list at the time when statement is encountered
- `$monitor` : Whenever there is a change in any argument, displays the entire list at end of time step

## Simulation Control Task

- `$finish` : makes the simulator to exit
- `$stop` : suspends the simulation

## Time

- `$time`: gives the simulation

# TYPE OF PORT CONNECTIONS

```
C module child_mod (sig_a, sig_b,  
    sig_c, sig_d);  
    input    sig_a, sig_b;  
    output   sig_c, sig_d;
```

```
    // module description goes here.
```


```
endmodule
```

---

```
module parent_mod;  
    wire [4:0] g;
```

```
    child_mod G1 (g[3], g[1], g[0], g[2]);
```
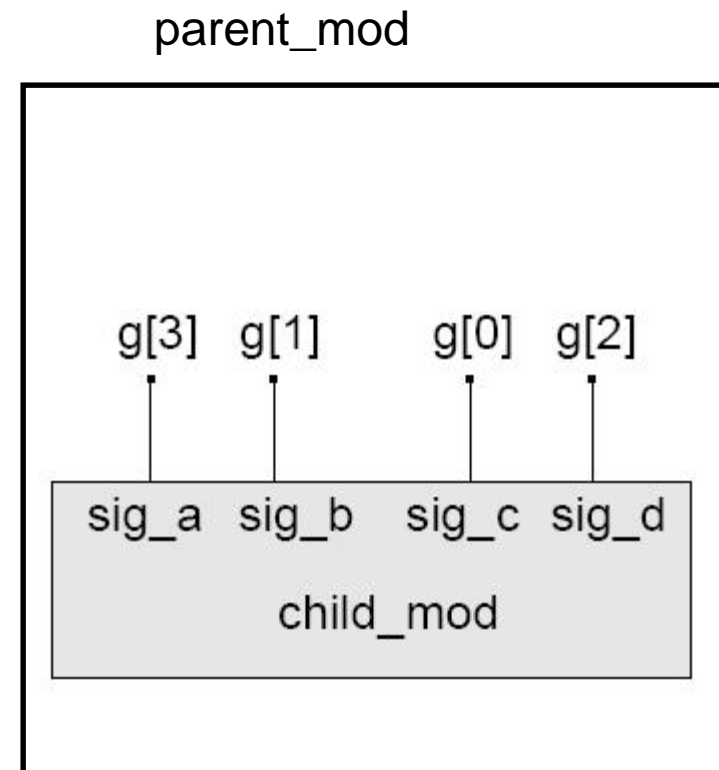
```
    // Listed order is significant  
endmodule
```





# TYPE OF PORT CONNECTIONS (CONT.)

```
module child_mod (sig_a, sig_b,  
( sig_c, sig_d);  
  input      sig_a, sig_b;  
  output     sig_c, sig_d;
```

```
  // module description goes here.
```


```
endmodule
```

---

```
module parent_mod;  
  wire [3:0] g;  
  // Listed order not significant
```

```
  child_mod G1 ( .sig_c(g[3]),  
                 .sig_d(g[2]),  
                 .sig_b(g[0]),  
                 .sig_a(g[1]));
```

```
endmodule
```

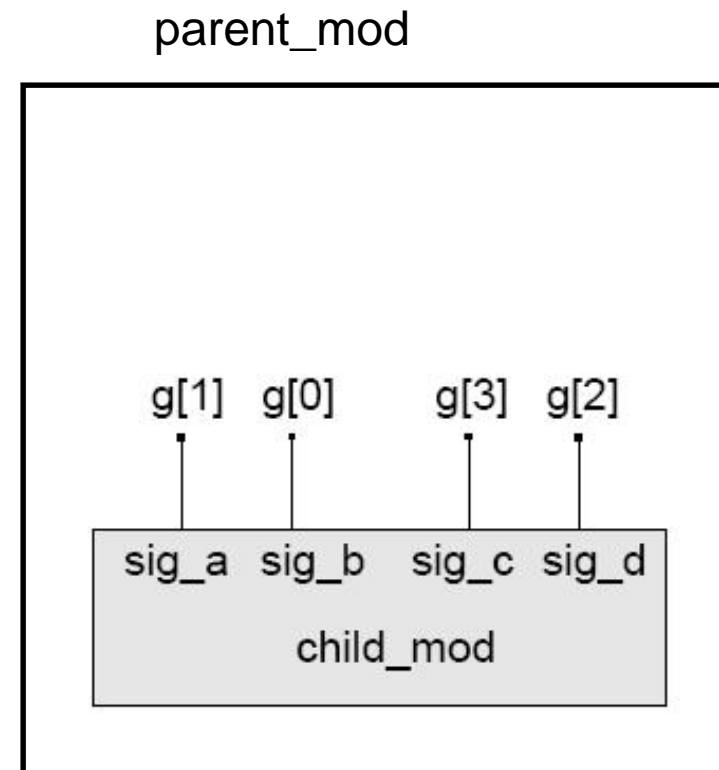

# EMPTY PORT CONNECTIONS

If an input port of an instantiated module is empty, the port is set to a value of z (high impedance).

<pre>module child_mod(In1, In2, Out1, Out2)   input In1;   input In2;   output Out1;   output Out2;   //behavior relating In1 and In2 to Out1 endmodule</pre>	<pre>module parent_mod(.....)    child_mod mod(A, ,Y1, Y2);   //Empty Input endmodule</pre>
---	---

If an output port of an instantiated module is left empty, the port is considered to be unused.

```
module parent_mod(.....)


  child_mod mod(A, B, Y1, ); //Empty Output
endmodule
```

# TEST BENCH

```
'timescale 1ns/100ps
module Top;
    reg PA, PB;
    wire PSum, PCarry;

    HalfAdder G1(PA, PB, PSum, PCarry);

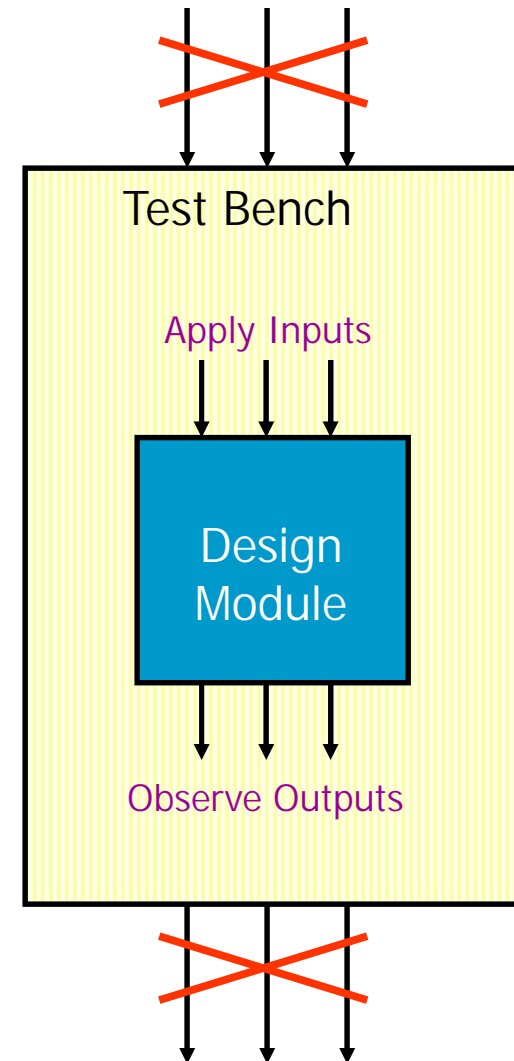    initial begin: LABEL
        reg [2:0] i;
        for (i=0; i<4; i=i+1) begin
            {PA, PB} = i;
            #5 $display ("PA=%b PB=%b
PSum=%b PCarry=%b", PA, PB, PSum,
PCarry);
        end // for
    end // initial
endmodule
```



# TEST BENCH - GENERATING STIMULUS

**Example: A sequence of values**

**initial begin**


Clock = 0;

#50 Clock = 1;

#30 Clock = 0;


#20 Clock = 1;

**end**

 

# TEST BENCH - GENERATING CLOCK

## Repetitive Signals (clock)

 

## A Simple Solution:

**wire** Clock;

**assign** #10 Clock = ~ Clock

## Caution:

- Initial value of Clock (**wire** data type) = z
- $\sim z = x$  and  $\sim x = x$

# TEST BENCH - GENERATING CLOCK (CONT.)

## Initialize the Clock signal

```
initial begin
    Clock = 0;
end
```

**Caution: Clock is of data type wire, cannot be used in an initial statement**

**Solution:**

```
reg Clock;
...
initial begin
    Clock = 0;
end
...
always begin
    #10 Clock = ~ Clock;
end
```

forever loop can  
also be used to  
generate clock

# DESIGN ENTRY METHODS

**Depending on the design complexity & functionality a digital logic block can**

**be represented by using one of the following approaches:**

**1. RTL Coding using HDL (i.e VHDL/Verilog HDL etc.)**

**2. Truth Table representation**

**3. State Diagram**

**4. Flow chart**

**5. Block diagram**

# FUNCTIONAL SIMULATION

**Functional emulation of a circuit design through software programs is Simulation.**

**It is the process of applying stimuli to a model over time and producing corresponding responses from the model**

**Simulation is used for design verification:**

- Validate assumptions
- Verify logic
- Verify performance (timing)



# STEPS IN SIMULATION

## **Compilation :**

- **Checks VHDL source code for syntax and semantic rules of VHDL.**
- **If a syntax or semantic error occurs then the compiler gives an error message.**

## **Elaboration :**

- **Ports are created for each instance of component**
- **Memory storage is allocated for each required signals**
- **Interconnections among the port signals are specified**
- **Executes VHDL processes/ Verilog constructs in proper sequence mechanism**

# STEPS IN SIMULATION

## **Initialization :**

**Here initial values present in the declaration statement are assigned to either signals or variables.**

## **Execution :**

**Here simulator accepts simulation commands like (run, assign, watch) ,which controls the simulation of the system and specify desired output.**

**Every process is executed until it suspends and signal values are updated after the process suspends.**

**Interconnections among the port signals are specified**

**Simulation ends when signals are updated with new values**

# TYPES OF SIMULATION

## Functional Simulation :

- Ignores timing aspects.
- Verifies only the functionality of the design

## Behavioral Simulation :

- Given functionality is modeled using HDLs.
- Timing aspects are considered.  
Example :  $f \leq a$  and b after 5ns.

## Gate level Simulation :

- Its used to check the Timing performance of a design.
- Delay parameters of Logic cells are used to verify timings
- Gate delays are vendor specific.


# SYNTHESIS

**“ Synthesis process converts user’s Hardware description into structural logic description.**

**Synthesis provides a means to convert schematics or HDL into real-world hardware.**


**Synthesis tools convert the described hardware into a net list that a vendor may use to create the chip or board.**

# Logic Synthesis

 

 
# ASIC & FPGA Synthesis


$X = (a \text{ and } b) \text{ or } (c \text{ and } d) ;$



Generic

 

ASIC

 

FPGA

# SYNTHESIS – DESIGN FLOW


**Synthesis and Optimization processes generate a gate level net list for the target technology.**

**This net list can be optimized under various constraints, such as area or speed.**

**Synthesis process is as follows:**

- Input data is transformed into a description based on Boolean Equations.
- A Technology independent logic level optimization based upon the Boolean Equations is performed by applying rules of Boolean Algebra.
  - **This eliminates redundant logic and reduces the area requirement or delay of the circuit.**
  - **Logic level optimization is split into phases:**
    - **Flattening and Structuring.**


# SYNTHESIS PROCESS

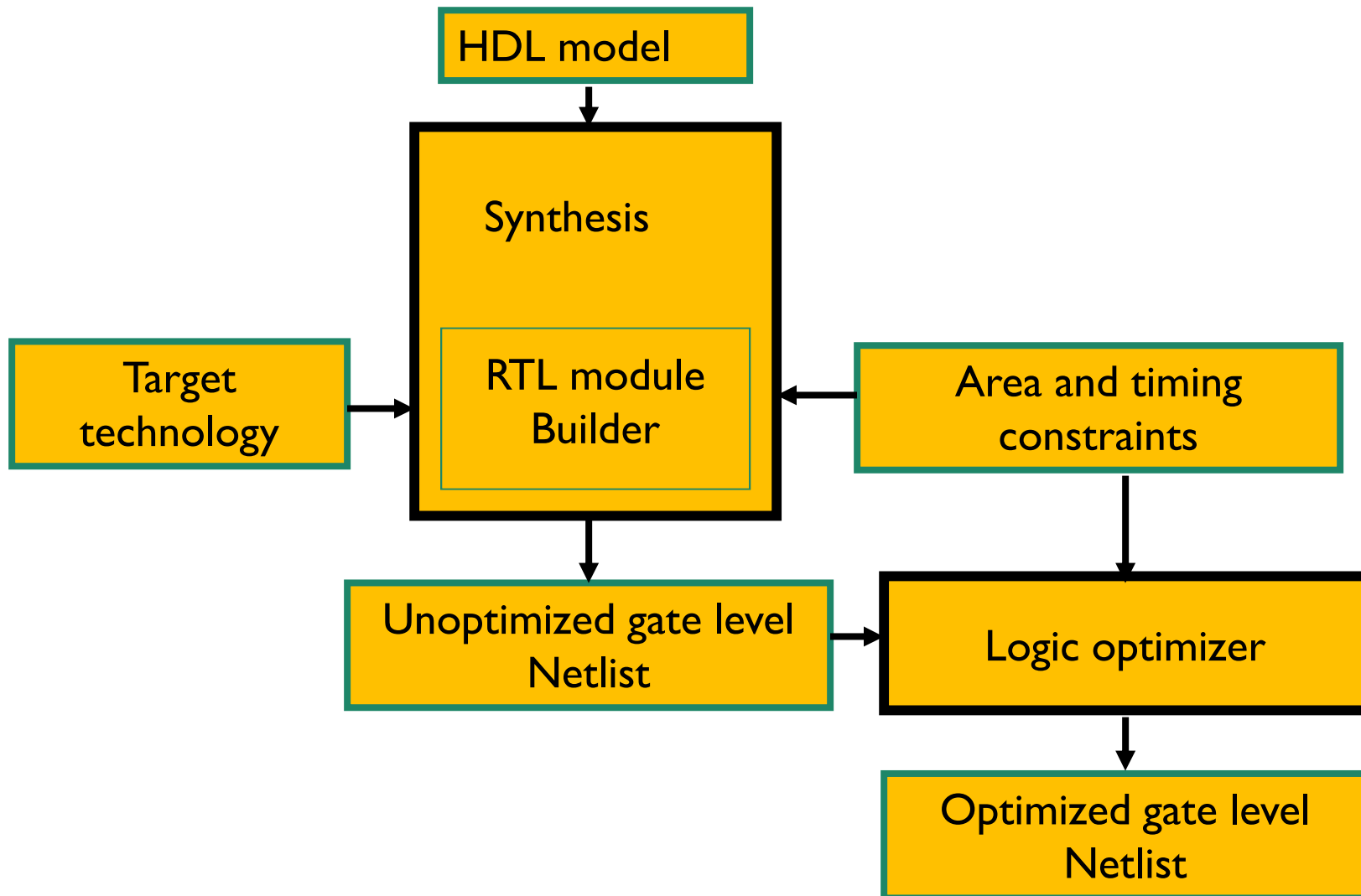



# SYNTHESIS CONSTRAINTS

Synthesis constraints

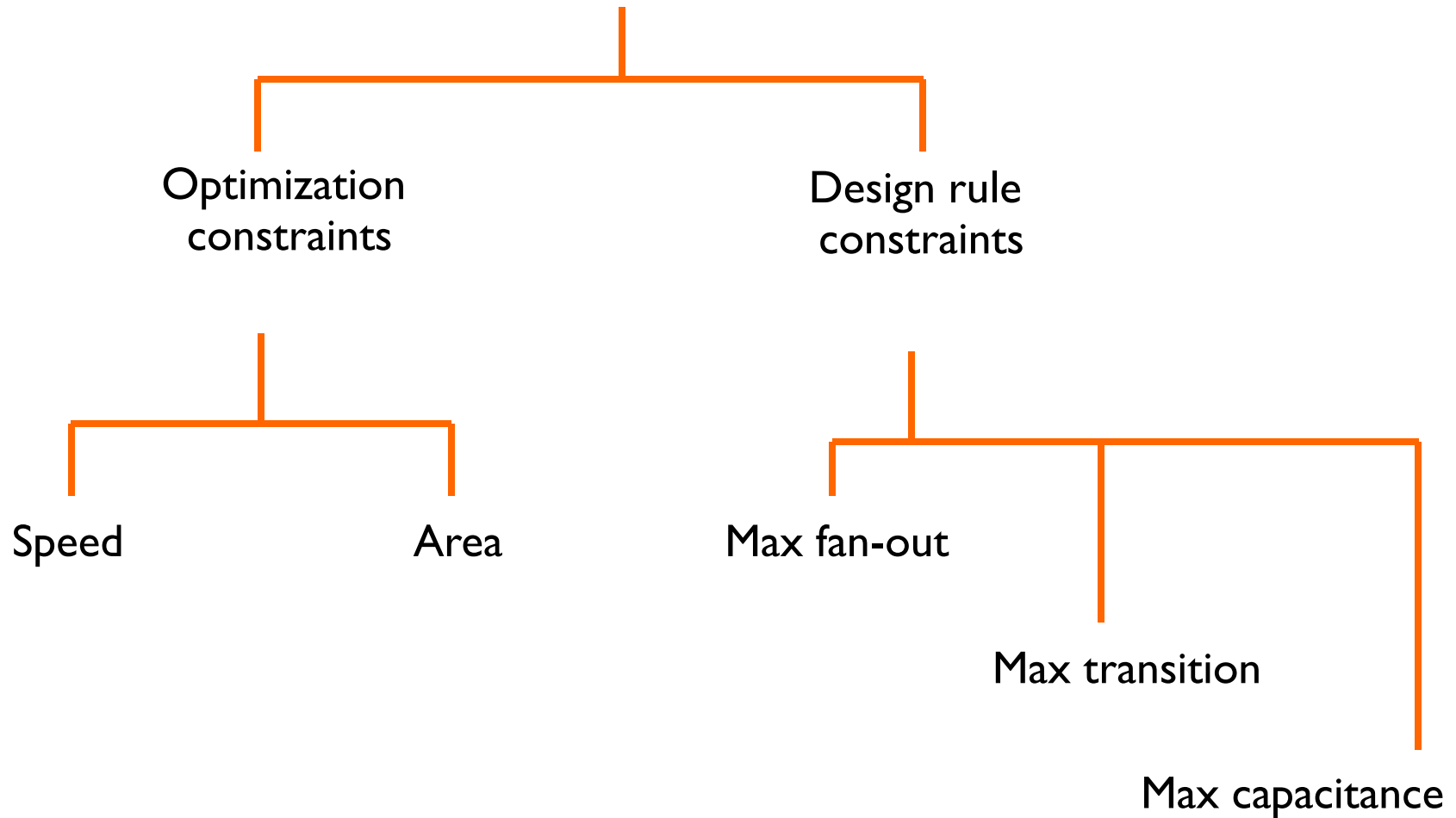

# SYNTHESIS ADVANTAGES

**Synthesis is constraint driven :**

**-It meets design criteria of Timing , Size , and Power.**

- ☐ **A synthesized design can be re synthesized into new technologies.**
- ☐ **Forces higher levels of Abstraction.**
- ☐ **Leads to ease in debugging and code Portability.**
- ☐ **Enables designer to focus on larger design goals, as it is easier to relate RTL to hardware.**

# SYNTHESIS TOOLS - FEATURES

**Synthesis tools should provide features such as**

- Control over Critical Path Synthesis.
- Remove all false paths.
- Resource Sharing of Adders, Incrementers, Decrementers, and multipliers.
- Automatic RAM Inference.
- Replicate logic to meet Fan out limitations.
- Remove unused logic , duplicate flip-flops etc.
- Provide optimization across Design Hierarchy.

# CODING FOR SYNTHESIS

**Good coding style means that the Synthesis tool can identify constructs within your code that it can easily map to technology features.**

**All programmable Devices may have its own unique architectural resources. For ex: Xilinx Virtex series has inbuilt RAM.**

- Readymade codes(Macros) are provided by vendors which are optimized to the target technology  
Ex. LogiBlox in Xilinx

**Note:** For more information on coding guidelines for synthesizable HDL refer to:

## **HDL Coding guidelines**

**Reference:** <http://standards.ieee.org/getieee/1800/download/1800-2012.pdf>

# MODELING FOR SYNTHESIS

**Design methodology uses synthesis tool to convert RTL code to library cells**

- Code is interpreted & hardware created
  - Knowledge of FPGA architecture is helpful
- Synthesis tools require certain coding to generate correct logic
  - Subset of Verilog language supported
  - The goals of coding style are efficiency and predictability
- Initialization controlled by device

**Pre- & post-synthesis logic should operate the same**

# WRITING SYNTHESIZABLE VERILOG

- **Sensitivity lists**
- **Blocking vs. non-blocking**
- **Latches vs. registers**
- **if-else structures**
- **case statements**
- **Combinatorial loops**
- **Internally generated clocks**
- **Using functions and tasks**
- **Inferring logic functions**


# TWO TYPES OF PROCESSES

- **Combinatorial Process**

- Sensitive to all inputs used in the combinatorial logic

 **always @(a or b or sel)**

*sensitivity list includes all inputs used in the combinatorial logic*




- **Clocked Process**

- Sensitive to a clock or/and control signals

 **always @(posedge clk or negedge clr\_n)**

*sensitivity list does not include the **d** input, only the clock or/and control signals*



# SENSITIVITY LIST

**Incomplete sensitivity list in an always block may result in differences between RTL and gate-level simulations**

```
always @ (a or b)  
  y = a & b & c;
```

**Incorrect Way – the simulated behavior is not that of the synthesized 3-input AND gate**

```
always @ (a or b or c)  
  y = a & b & c;
```

**Correct way for the intended AND logic !**



# BLOCKING VS. NON-BLOCKING



**Recommendation: Use non-blocking assignments for clocked processes when writing synthesizable code**

# BLOCKING VS. NON-BLOCKING EXAMPLE

## Blocking (=)

```
Always @(posedge clk)
begin
    a = in;
    b = a;
    out = b;
end
```



Synthesized Result:

  

## Nonblocking (<=)

```
Always @ (posedge clk)
begin
    a <= in;
    b <= a;
    out <= b;
end
```

Synthesized Result:

  

# LATCHES VS. REGISTERS

**Latches are implemented using combinatorial logic & can make timing analysis more complicated**


## **Recommendations**

- Design with registers (RTL)
- Watch out for inferred latches
  - Latches inferred on combinatorial outputs when not results not specified for set of input conditions
 
# VARIABLE NOT INITIALIZED

Reading a data type object before it has been assigned a value infers a latch


```
always @ (i or a)
begin
    if (a == 1) val = val;
    else val = val + 1;
    case (val)
        1'b0 : q = i[0];
        1'b1 : q = i[1];
    endcase
end
```


 
# ASSIGNING INITIAL VALUE TO VARIABLE

Assigning a value to a data type object prior to reading it prevents a latch

```
always @ (i or a)
begin
    val = 1'b0;
    if (a == 1) val = val;
    else val = val + 1;
    case (val)
        1'b0 : q = i[0];
        1'b1 : q = i[1];
    endcase
end
```



# IF-ELSE STRUCTURE

**if-else structure implies prioritization and dependency**

**If sequential statements are mutually exclusive, individual if structures may be more efficient**

**When writing if and if-else structures**

- Cover all cases
  - Uncovered cases result in latches
- Assign values before reading data type object
  - Reading unassigned data type object results in latches
- For efficiency, consider assigning initial values and explicitly covering only those results different from initial values

# PRIORITIZATION & DEPENDENCY (IF-ELSE)

**Nested else if statements imply prioritization of and dependency in logic**

```
reg [4:0] state;  
parameter s0 = 5'h0, s1 = 5'h11, s2 = 5'h12, s3 = 5'h14, s4 = 5'h18;  
always @ (posedge clk or negedge reset_n) begin  
    if (reset_n == 0) state <= s0;  
    else begin  
        if (state == s0) begin  
            if (in == 1) state <= s1; else state <= s0;  
        end  
        else if (state == s1) state <= s2;  
        else if (state == s2) state <= s3;  
        else if (state == s3) state <= s4;  
        else if (state == s4) begin  
            if (in == 1) state <= s1; else state <= s0;  
        end  
    end  
end  
end
```

# PRIORITIZATION/DEPENDENCY REMOVED (IF-ELSE)

Individual if statements where logic is exclusive may be more efficient


```
reg [4:0] state;
parameters s0 = 5'h0, s1 = 5'h11, s2 = 5'h12, s3 = 5'h14, s4 = 5'h18;
always @ (posedge clk or negedge reset_n) begin
    if (reset_n == 0) state <= s0;
    else begin
        if (state == s0) begin
            if (in == 1) state <= s1; else state <= s0;
        end
        if (state == s1) state <= s2;
        if (state == s2) state <= s3;
        if (state == s3) state <= s4;
        if (state == s4) begin
            if (in == 1) state <= s1; else state <= s0;
        end
    end
end
end
```



# UNWANTED LATCHES – NESTED IF STATEMENTS

```
always @ (ina or inb)
begin
    if (ina == 1) begin
        if (inb == 1) out = 1;
        end
    else out = 0;
end
```

<u>ina</u>	<u>inb</u>	<u>out</u>
1	1	1
0	0	0
0	1	0
1	0	?

 


- Uncovered cases infer latches
  - no default value for data type objects

# UNWANTED LATCHES REMOVED – NESTED IF STATEMENTS

```
always @ (ina or inb)
begin
  if (ina == 1)
    begin
      if (inb == 1) out = 1;
      else out = 0;
    end
  else out = 0;
end
```

<u>ina</u>	<u>inb</u>	<u>out</u>
1	1	1
0	0	0
0	1	0
1	0	0

 

- All cases are covered; no latch inferred

# INEFFICIENT CASE STATEMENT

```
reg [4:0] state;
parameter s0 = 5'b00000, s1 = 5'b10001,
           s2 = 5'b10010, s3 = 5'b10100,
           s4 = 5'b11000;
always @ (posedge clk or negedge reset_n) begin
    if (reset_n == 0) state <= s0;
    else
        case (state)
            s0:    if (in == 1) state <= s1;
                   else state <= s0;
            s1:    state <= s2;
            s2:    state <= s3;
            s3:    state <= s4;
            s4:    if (in == 1) state <= s1;
                   else state <= s0;
        endcase
    end
```

# EFFICIENT CASE STATEMENT

```
reg [4:0] state;
parameter  s0 = 5'b00000,      s1 = 5'b10001,
            s2 = 5'b10010,      s3 = 5'b10100,
            s4 = 5'b11000;
always @ (posedge clk or negedge reset_n) begin
  if (reset_n == 0) state <= s0;
  else
    case (state)
      s0:      if (in == 1) state <= s1;
                else state <= s0;
      s1:      state <= s2;
      s2:      state <= s3;
      s3:      state <= s4;
      s4:      if (in == 1) state <= s1;
                else state <= s0;
      default: state <= s0;
    endcase
end
```

**All 32 cases covered**

**A case structure where all cases are covered will typically synthesize most efficiently**

# "FULL" CASE

All possible case-expression binary patterns can be matched to a case item or a case default

Non-full case statements infer latches

Adding "full\_case" synthesis directive to non-full case statements may cause pre-synthesis and post-synthesis simulation mismatch

## Mismatched Code

```
always @ (ena or a) begin
    out = 2'b00;
    case ({ena,a}) //synthesis full_case
        2'b1_0: out[a] = 1'b1;
        2'b1_1: out[a] = 1'b1;
    endcase
end
```

## Full Statement

```
always @ (ena or a) begin
    out = 2'b00;
    case ({ena,a})
        2'b1_0: out[a] = 1'b1;
        2'b1_1: out[a] = 1'b1;
        default: out = 2'b00;
    endcase
end
```

## “PARALLEL” CASE

Only possible to match a case expression to one and only one case item

Non-parallel case statements infer priority encoders

Adding “parallel\_case” synthesis directive to non-parallel case statement may cause mismatch between Verilog functional model and synthesized logic

# "FULL CASE" & "PARALLEL CASE" DIRECTIVES

## **Don't use!**

- Code synthesizable case statements to be "full" and "parallel" when designing

## **Great paper discusses the perils of CASE synthesis directives**

- [http://www.sunburst-design.com/papers/CummingsSNUG1999Boston\\_FullParallelCase.pdf](http://www.sunburst-design.com/papers/CummingsSNUG1999Boston_FullParallelCase.pdf)

# COMBINATIONAL LOOPS


**Common cause of instability**

**Behavior of loop depends on the relative propagation delays through logic**

- Propagation delays can change

**Simulation tools may not match hardware behavior**

 **All feedback loops should include registers**





# INTERNALLY GENERATED CLOCKS

**Can lead to both functional and timing problems**

**If you must have internally generated clocks,  
proper design considerations required**

- Keep the clock generation circuitry as a separate module at top level of the design
- Always register the output of combinational logic before using it as a clock

**Recommendation: Use FPGA PLL megafunction  
for gated clocks**

# USING FUNCTIONS & TASKS

**Functions and tasks can be used in synthesized modules**

- Variables in functions must be local

**Make generic if possible for reusability**

```
// function for ...  
  
function ['BUS_WIDTH-1:0] out;  
input a;  
integer a;  
begin  
    // ... Code for function goes here  
end  
endmodule
```

# INFERRING LOGIC FUNCTIONS

## **Using behavioral modeling to describe logic blocks**

- e.g. Latches, registers, counters, tri-states, memory, arithmetic

## **Synthesis tools recognize description & insert logic functions**

- Functions typically pre-optimized for utilization or performance

## **Makes code vendor-independent**

# BIDIRECTIONAL PINS

```
module module_name (... , bidir, ...);
```

```
inout bidir;
```

```
wire incoming_signal;
```

```
assign incoming_signal = bidir;
```

*logic operating on incoming\_signal*  
*logic generating outgoing\_signal*

```
assign bidir = oe ? outgoing_signal : 1'bZ;
```

- *Declare Pin As Direction*  
**inout**
- *Use inout As Both Input & Tri-State Output*

*bidir as an input*

*bidir as an tri-stated output*

# INFERRING LATCHES

```
module latches (d, gate,q);
```

```
input d, gate ;
```

```
output reg q ;
```

```
wire d, gate ;
```

```
always @(d or gate)
```

```
if (gate)
```

```
q <= d ;
```

```
endmodule
```



*sensitivity list includes both inputs*


*level sensitive...not edge*

*What happens if gate = '0'?*

⇒ **Implicit Memory & Feedback**
 
# INFERRING FLIP-FLOPS

```
module dff_1(clk, d, clr_n, pre, q);  
input clk, d, clr_n, pre;  
output reg q;  
  
always @(posedge clk or negedge clr_n)  
    if (clr_n == 0)  
        q <= 0;  
    else  
        q <= d;  
endmodule
```



– Simple register logic


# INFERRING FLIP-FLOPS

```
module dff_1(clk, d, clr_n, pre, q);  
input clk, d, clr_n, pre;  
output reg q;
```

```
always @(posedge clk or negedge clr_n)  
    if (clr_n == 0)
```

```
        q <= 0;  
    else  
        if (pre == 1)  
            q <= 1;  
        else  
            q <= d;
```


```
endmodule
```

 

- This implements asynchronous clear and synchronous preset control signals for the register
- Use Non-blocking Assignment
- Synchronous controls are not included in sensitivity list
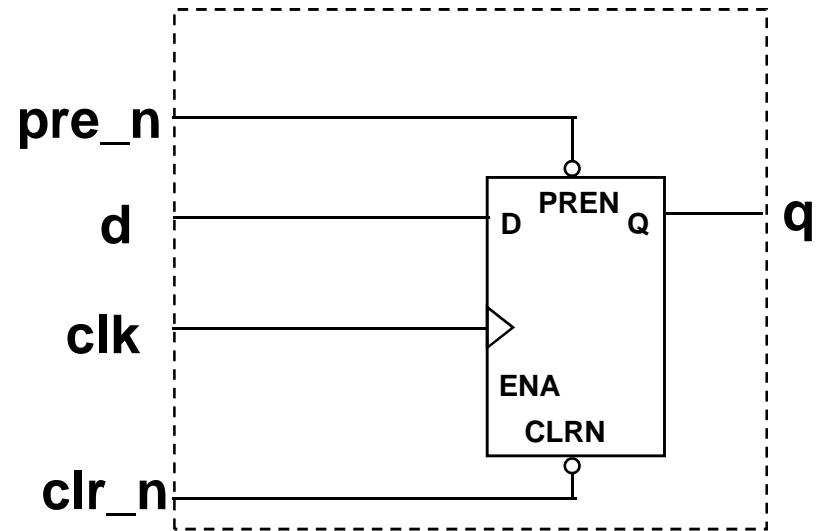
# DFF WITH ASYNC CLEAR & PRESET

```
module dff_1(clk, d, clr_n, pre_n, q);  
input clk, d, clr_n, pre_n;  
output reg q;  
  
always @(posedge clk or negedge clr_n  
or negedge pre_n)  
    if (clr_n == 0)  
        q <= 0;  
    else if (pre_n == 0)  
        q <= 1;  
    else  
        q <= d;  
endmodule
```



- 2 Asynchronous Controls
- Do the Registers in the Hardware Have Both Ports?
- How Does Hardware Behave?  
Does Preset or Clear Have Priority If Both Asserted?




# CONTROL SIGNAL PRIORITY

1. **Asynchronous clear (aclr)**
2. **Asynchronous preset (pre)**
3. **Asynchronous load (aload)**
4. **Enable (ena)**
5. **Synchronous clear (sclr)**
6. **Synchronous load (sload)**
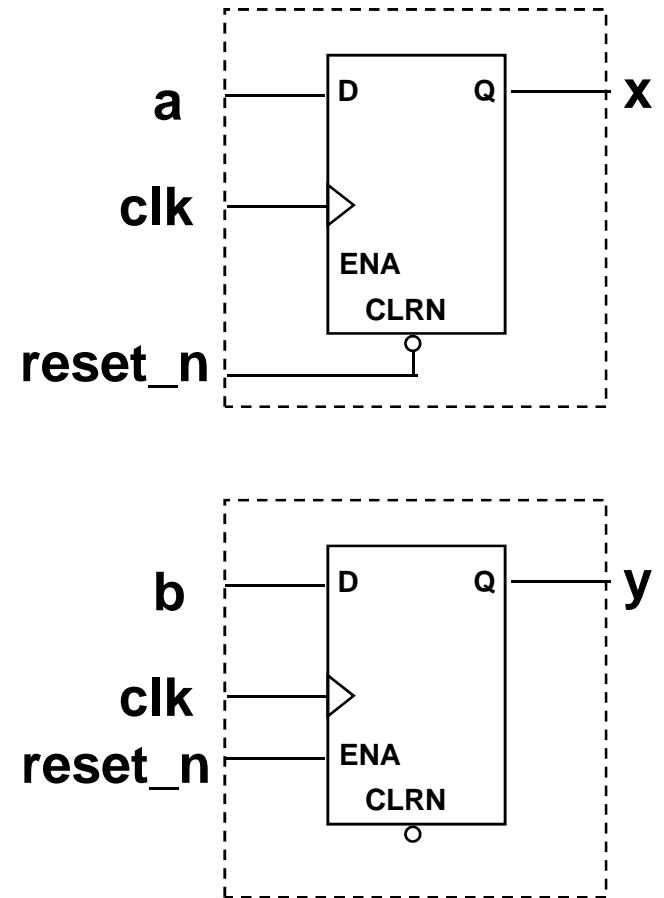
# INCORRECT CONTROL LOGIC


```
module dff_1(clk, reset_n, a, b, x, y);  
input clk, reset_n, a, b;  
output reg x, y;  
  
always @(posedge clk or negedge reset_n)  
    if (reset_n == 0)  
        x <= 0;  
    else begin  
        x <= a;  
        y <= b;  
    end  
endmodule
```

- *y* Is Not Included in Reset Condition
- **reset** Clears **x** but Acts More Like an Enable for **y**


 
# DFF WITH CLOCK ENABLE

```
module dff_1(clk, d, q, ena, clr_n);  
input clk, d, ena, clr_n;  
output reg q;  
  
always @(posedge clk or negedge clr_n)  
    if (clr_n == 0)  
        q <= 0;  
    else if (ena == 1)  
        q <= d;  
endmodule
```




- If the synthesis tool does not recognize this as an enable it will be implemented using extra LUTs
- Any other synchronous controls (e.g. *sclr*, *sload*) are nested underneath the enable test (i.e. use “if,” not “else if”)

# SHIFT REGISTERS

```
module shift(aclr_n, enable, shiftin, clock, q);  
input aclr_n, enable, shiftin, clock;  
output reg [7:0] q;
```

```
always @(posedge clock or negedge aclr_n)  
    if (aclr_n == 0)  
        q[7:0] <= 0;  
    else if (enable)  
        q[7:0] <= {q[6:0], shiftin};  
endmodule
```

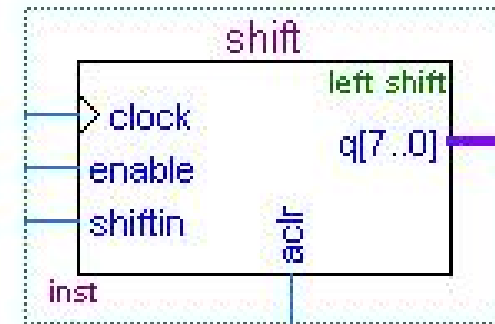- Shift register with parallel output, serial input, asynchronous clear and enable which shifts left
- Add or remove synchronous controls in a similar manor to previous slides




*Shift function*

- Use { , } for concatenation

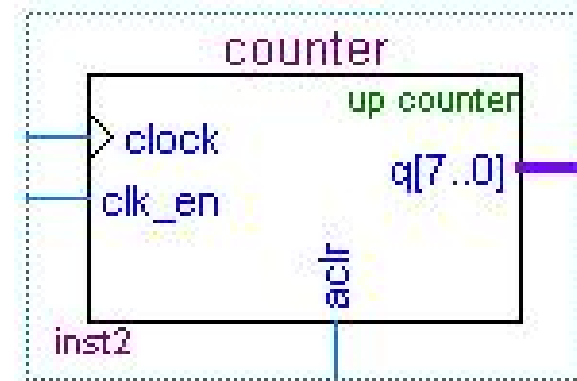
# COUNTER W/CLOCK ENABLE

```
module count(clk, ena, aclr_n, q);  
input clk, aclr_n, ena;  
output reg [7:0] q = 0;  
always @(posedge clk or negedge aclr_n)  
    if (aclr_n == 0)  
        q[7:0] <= 0;  
    else if (ena)  
        q <= q + 1;  
endmodule
```


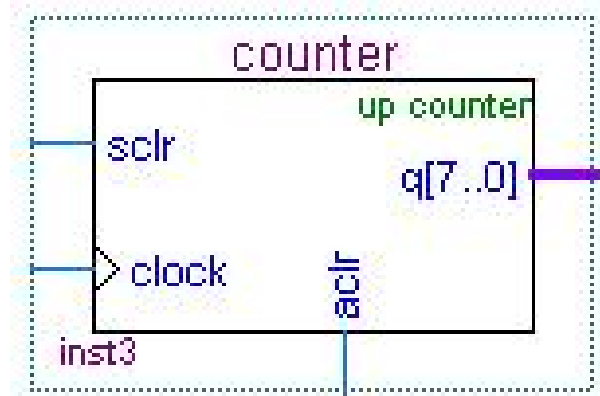
# COUNTER W/SYNCH AND ASYNCH CLEAR


```
module count(clk, sclr_n, aclr, q);  
input clk, aclr, sclr_n;  
output reg [7:0] q = 0;  
always @(posedge clk or negedge aclr_n)  
    if (aclr_n == 0)  
        q[7:0] <= 0;  
    else if (sclr_n)  
        q[7:0] <= 0 ;  
    else  
        q <= q + 1;  
endmodule
```


 
# UP/DOWN COUNTER W/SYNC LOAD

```
module count(clk, updown, aclr_n, sload, data, q);
input clk, aclr_n, updown, sload;
input [7:0] data;
output reg [7:0] q = 0;

always @(posedge clk or negedge aclr_n) begin
    if (aclr_n == 0)
        q[7:0] <= 0;
    else if (sload == 1)
        q <= data;
    else begin
        q <= q + (updown ? 1 : -1);
    end
end
endmodule
```



# MEMORY

**Synthesis tools have different capabilities for recognizing memories**

**Synthesis tools are sensitive to certain coding styles in order to recognize memories**

- Usually described in the tool documentation

**Tools may have limitations in architecture implementation**

- Newer FPGA devices support synchronous writes only
- Limitations in clocking schemes

**Must declare an array data type to hold memory values**



# INFERRED SINGLE-PORT MEMORY (1)

```
module ram(q, a, d, we, clk);
```

```
output reg [7:0] q;
```

```
input [7:0] d;
```

```
input [6:0] a;
```

```
input we, clk;
```

```
reg [6:0] read_add;
```

```
reg [7:0] mem [127:0];
```

```
always @(posedge clk) begin
```

```
  if (we)
```


```
    mem[a] <= d;
```

```
  read_add <= a;
```

```
end
```

```
assign q = mem[read_add];
```

```
endmodule
```

 

- Code describes a **128 x 8 RAM** with synchronous write & asynchronous read

# INFERRED SINGLE-PORT MEMORY (2)

```
module ram(q, a, d, we, clk);  
output reg [7:0] q;  
input [7:0] d;  
input [6:0] a;  
input we, clk;  
  
reg [6:0] read_add;  
reg [7:0] mem [127:0];  
  
always @(posedge clk) begin  
    if (we)  
        mem[a] <= d;  
        read_add <= a;  
        q <= mem[read_add];  
  
end  
  
endmodule
```

– Code describes a **128 x 8 RAM** with synchronous write & synchronous read



# INSTANTIATING LOGIC FUNCTIONS

**Using structural modeling to build logic**

**Synthesis tools replace structure with pre-built logic functions**

**Makes code insensitive to coding style**

# MOORE STATE MACHINES


**Outputs Are a Function of the States Only**

**Settle to their Final Values a Few Gate Delays After the Active Clock Edge**


**Outputs will be Constant for the Remainder of the Clock Period, Even if Inputs Happen to Change During the Clock Period**

**Isolates the Outputs from the Inputs**

# MOORE – BLOCK DIAGRAM

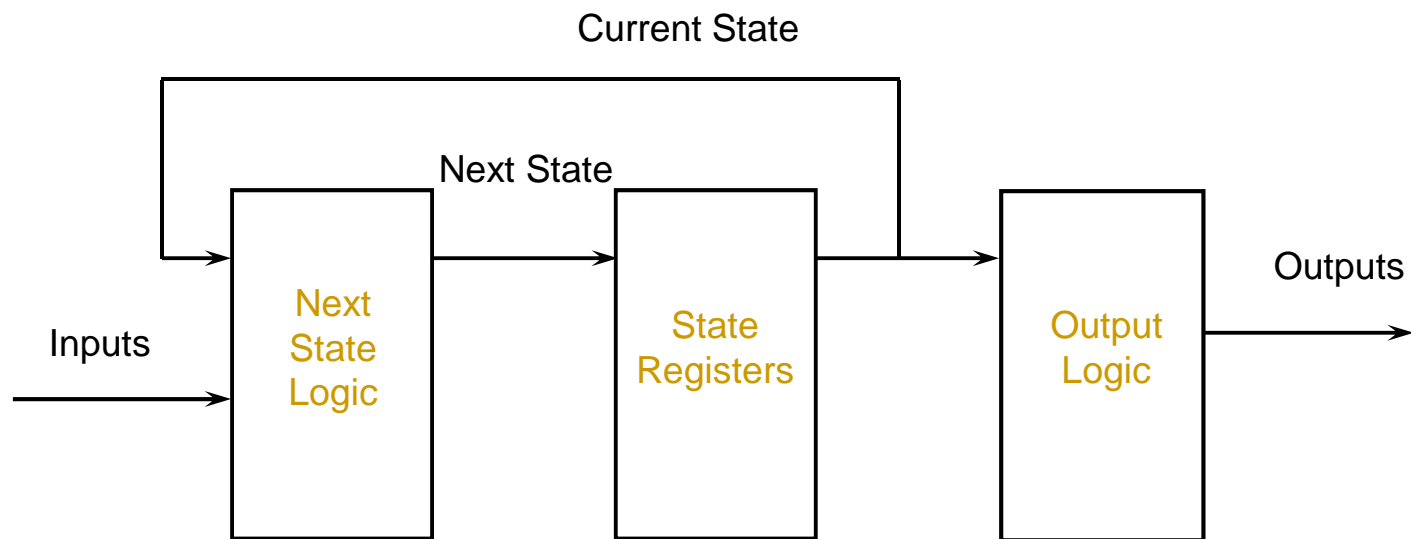

# MOORE – STATE DIAGRAM

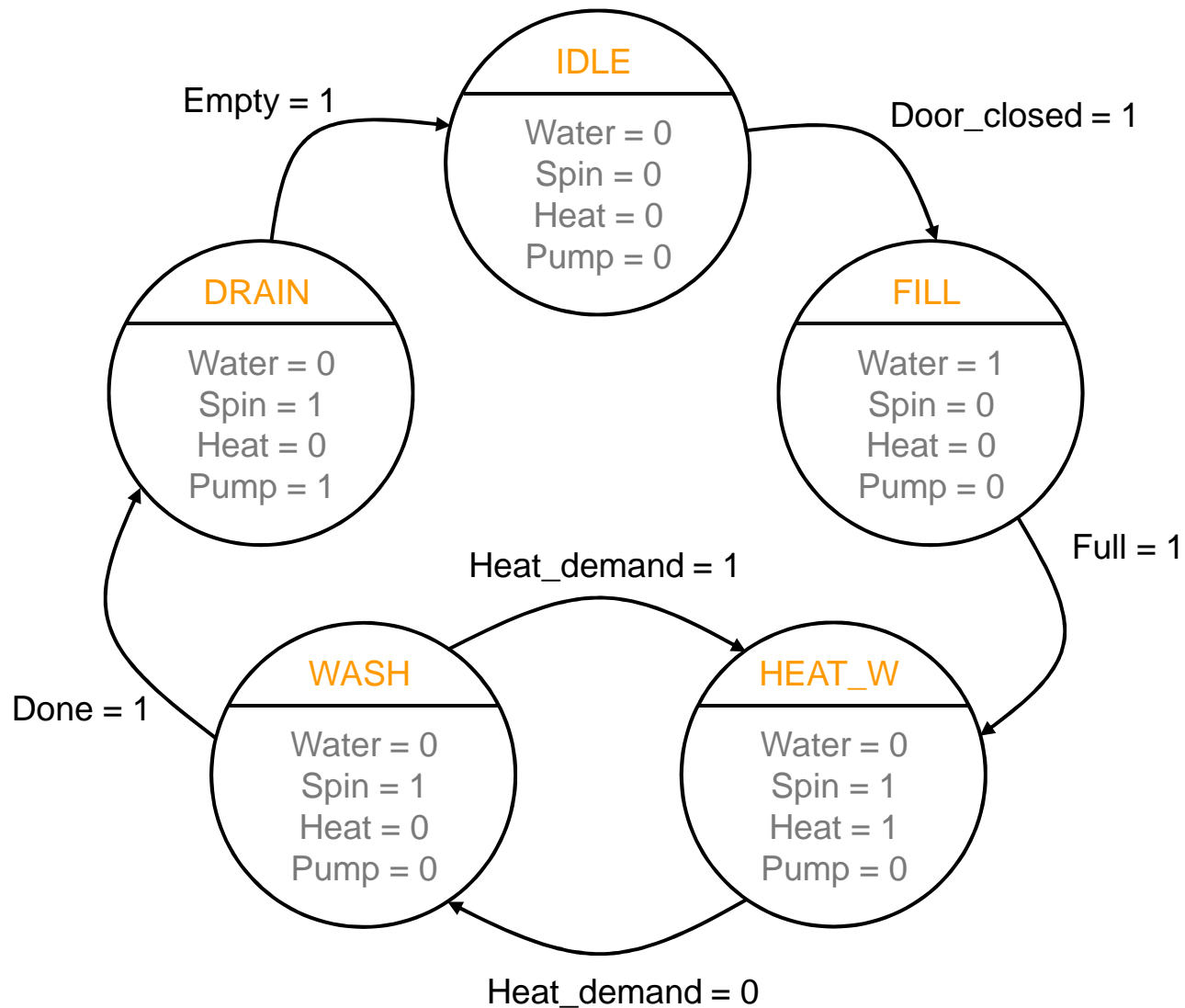

## INPUTS

Door\_closed  
Full  
Heat\_demand  
Done  
Empty

## OUTPUTS

Water  
Spin  
Heat  
Pump

# MEALY STATE MACHINES


**Outputs are a Function of the Inputs as well as the States**

**An Output May Change in the Middle of a Clock Period if an Input Changes**

**Output May Not be Consistent Throughout a Clock Cycle**

**However, Allows the Outputs to Follow Spurious Input Changes**


# MEALY – BLOCK DIAGRAM

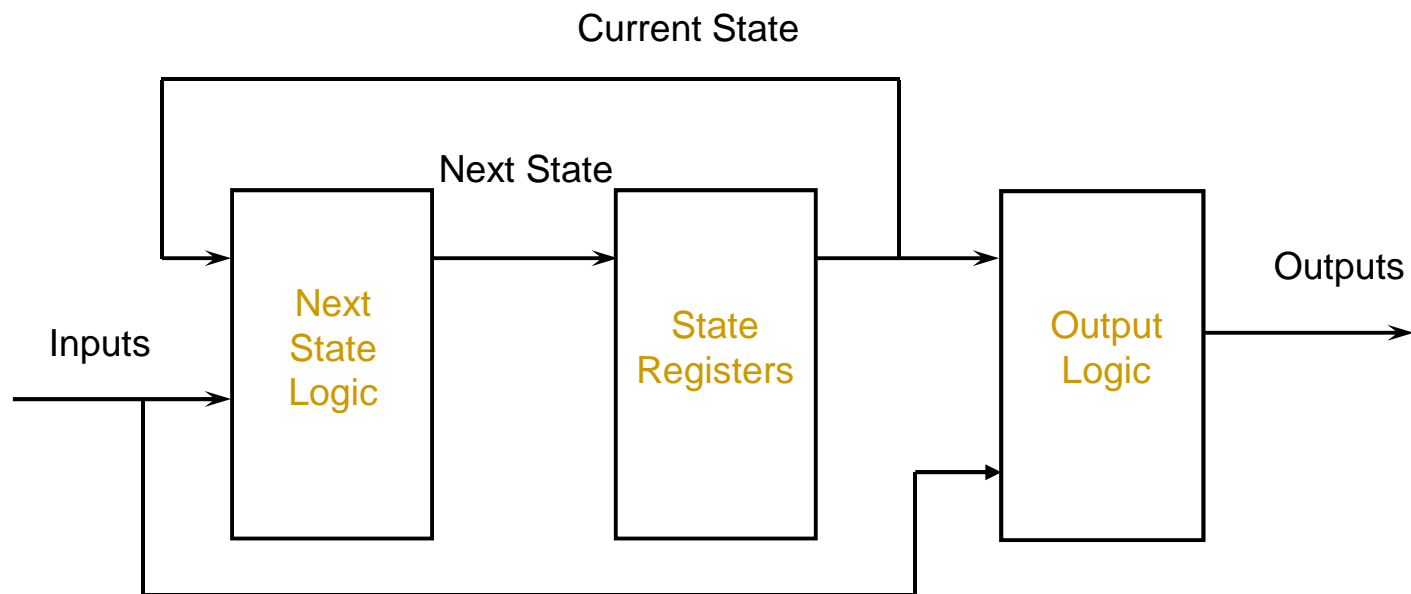



# MEALY – STATE DIAGRAM

## Mealy Often Leads to Fewer States

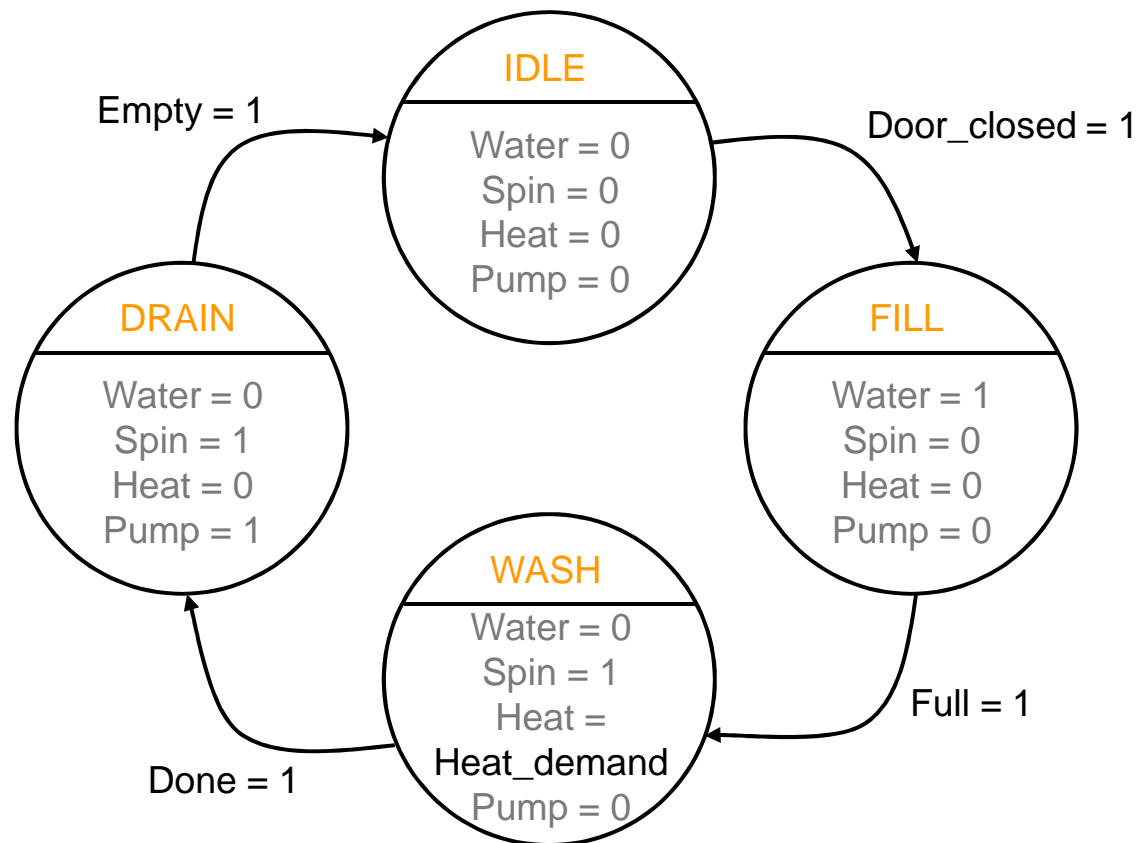

### INPUTS

Door\_closed  
Full  
Heat\_demand  
Done  
Empty

### OUTPUTS

Water  
Spin  
Heat  
Pump

# STATE MACHINE CODING

## Parameters used to define states

`parameter idle=0, fill=1, heat_w=2, wash=3,  
drain=4;`

- Parameter “values” are replaced with state encoding values as chosen by synthesis tool
  - Use options/constraints in synthesis tool to control encoding style (e.g. binary, one-hot, safe, etc.)
- ‘define statements also supported

## Registers are used to store state


`reg [2:0] state, next_state;`

## Use CASE statement to do the next-state logic, instead of IF-THEN statement

- Some synthesis tools recognize CASE statements for implementing state machines
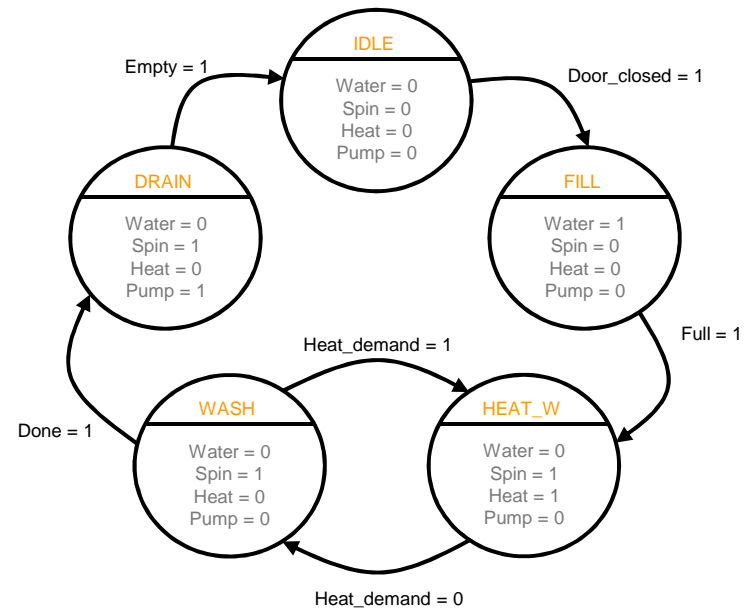
# STATE DECLARATION

```
module state_machine (clk, reset, door_closed,  
    full, heat_demand, done, empty,  
    water, spin, heat, pump);  
input clk, reset, door_closed, full, heat_demand,  
    done, empty;  
output reg water, spin, heat, pump;  
  
reg [2:0] state, next_state;  
  
parameter idle=0, fill=1, heat_w=2, wash=3,  
    drain=4;
```



States

State Registers

# NEXT STATE LOGIC

//Next State logic

always @(state or reset or door\_closed or full or  
heat\_demand or done or empty)

begin

next\_state = state; //default condition

case (state)

idle: if (door\_closed) next\_state = fill;

fill: if (full) next\_state = heat\_w;

heat\_w: if (heat\_demand == 0) next\_state = wash;

wash: begin

if (heat\_demand) next\_state = heat\_w;

if (done) next\_state = drain;


end

drain: if (empty) next\_state = idle;

default: next\_state = idle;

endcase

end

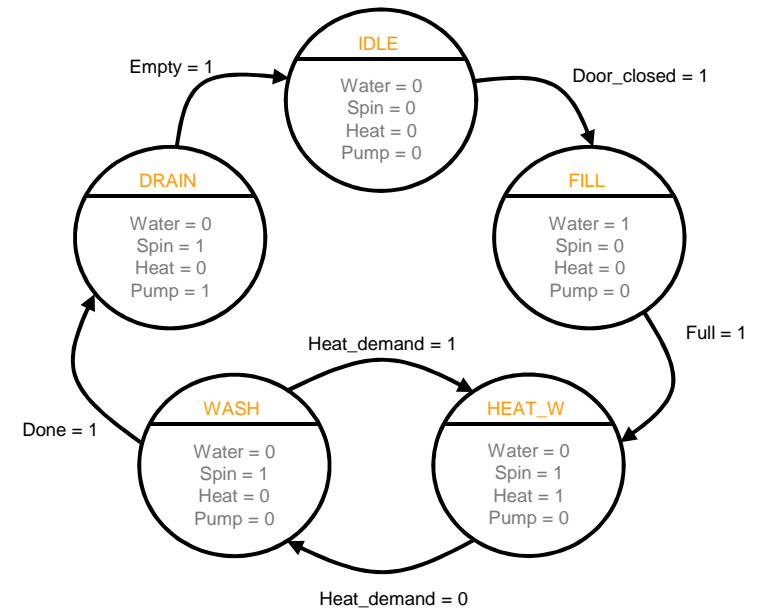


# USING TWO PROCESSES

## //State transitions

```
always @(posedge clk)
    state <= next_state;
```
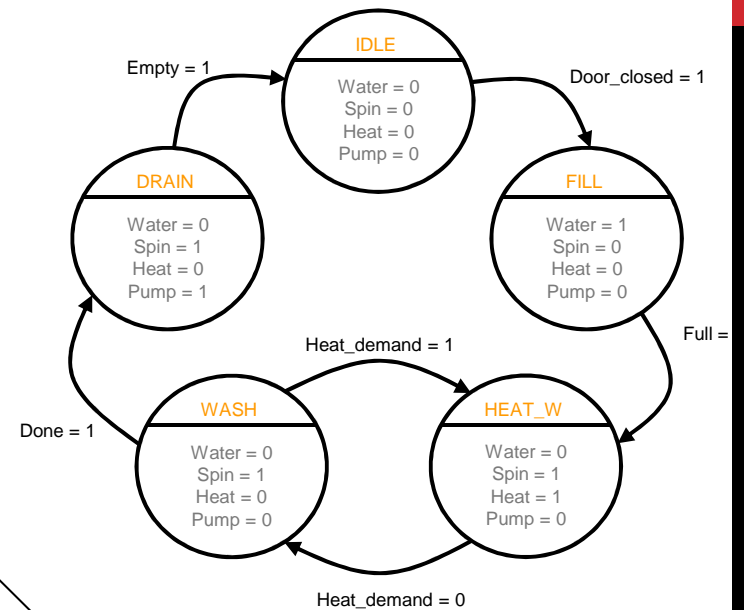
## //Next State logic

```
always @(state or reset or door_closed or full or
    heat_demand or done or empty)
begin
    next_state = state; //default condition
    case (state)
        idle: if (door_closed) next_state = fill;
        fill: if (full) next_state = heat_w;
        heat_w: if (heat_demand==0) next_state = wash;
        wash: begin
            if (heat_demand) next_state = heat_w;
            if (done) next_state = drain;
        end
        drain: if (empty) next_state = idle;
        default: next_state = idle;
    endcase
end
```



*State transitions*

*Next state logic*

# SYNCHRONOUS RESET

*Synchronous reset*

//State transitions

```
always @(posedge clk)
```

```
  if (reset)
```

```
    state <= idle;
```

```
  else
```

```
    state <= next_state;
```

//Next State logic

```
always @(state or reset or door_closed or full or
  heat_demand or done or empty)
```

```
begin
```

```
  next_state = state; //default condition
```

```
  case (state)
```

```
    idle: if (door_closed) next_state = fill;
```

```
    fill: if (full) next_state = heat_w;
```

```
    heat_w: if (heat_demand==0) next_state = wash;
```

```
    wash: begin
```

```
      if (heat_demand) next_state = heat_w;
```

```
      if (done) next_state = drain;
```


```
    end
```

```
    drain: if (empty) next_state = idle;
```

```
    default: next_state = idle;
```


```
  endcase
```

```
end
```

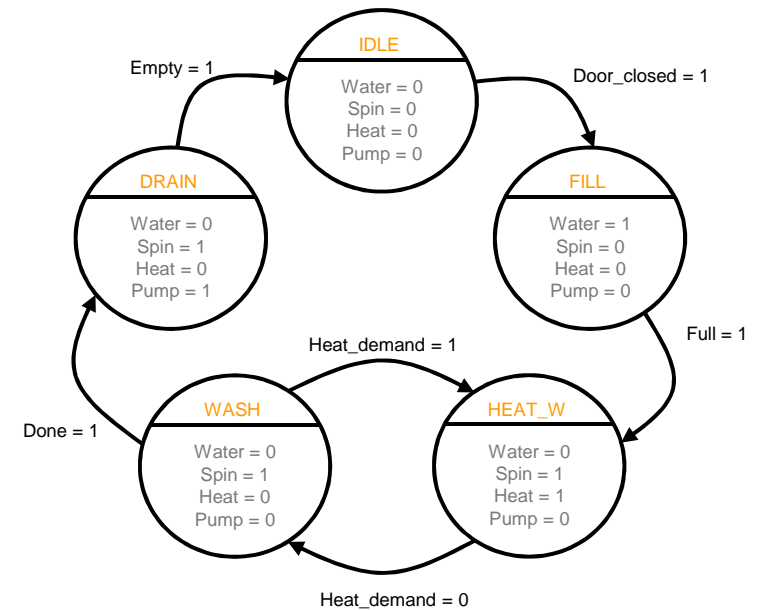
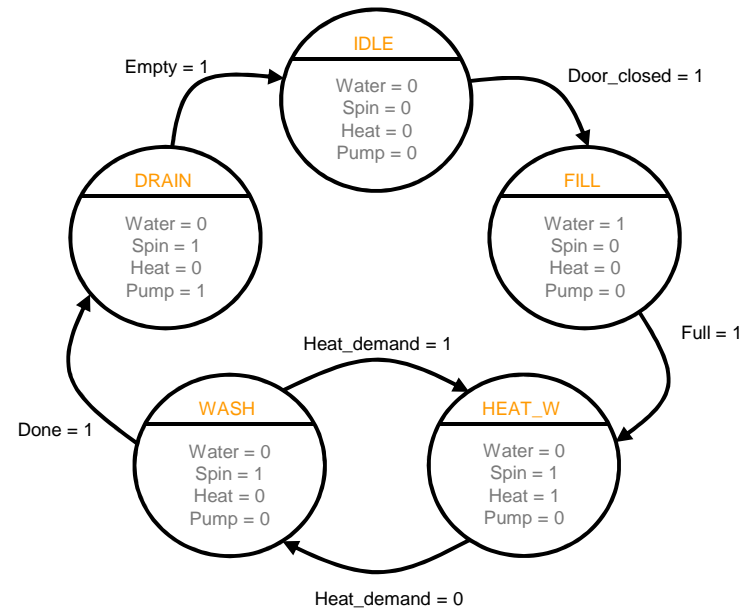
# COMBINATORIAL OUTPUTS


```
//output logic
always @(state)
begin
  water = 0;
  spin = 0;
  heat = 0;
  pump = 0;
  case (state)
    idle: ;
    fill: water=1;
    heat_w: begin spin =1; heat=1; end
    wash: spin =1;
    drain: begin spin =1; pump=1; end
  endcase
end
```



*Default output conditions*
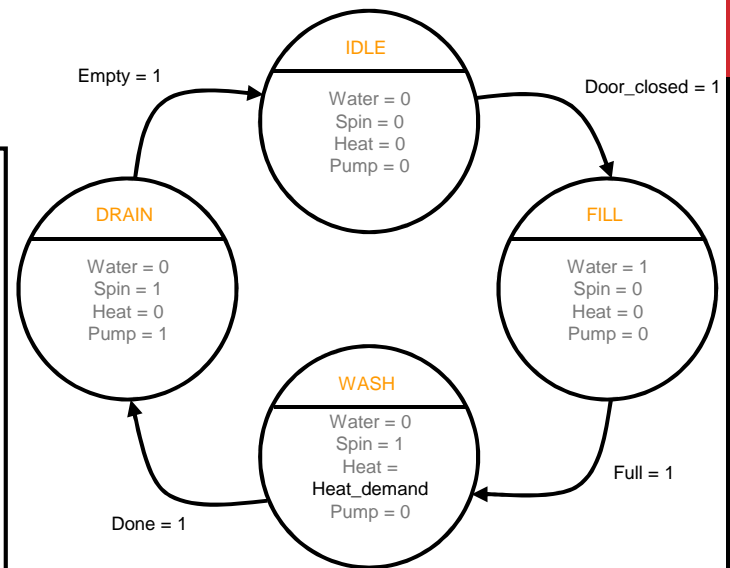
# MEALY COMBINATORIAL OUTPUTS

```
//output logic
always @(state)
begin
    water=0;
    spin=0;
    heat=0;
    pump=0;
    case (state)
        idle: ;
        fill: water=1;
        wash: begin spin =1; heat = heat_demand; end
        drain: begin spin =1; pump=1; end
    endcase
end
```



*Mealy Output*




# STATE MACHINE ENCODING STYLES

State	Binary Encoding	Grey-Code Encoding	One-Hot Encoding	Custom Encoding
Idle	000	000	00001	?
Fill	001	001	00010	?
Heat_w	010	011	00100	?
Wash	011	010	01000	?
Drain	100	110	10000	?
 
# MANUAL STATE ENCODING

```
module state_machine (clk, reset, door_closed,
    full, heat_demand, done, empty, water, spin, heat,
    pump);
input clk, reset, door_closed, full, heat_demand,
    done, empty;
output reg water, spin, heat, pump;

reg [2:0] state, next_state;
parameter idle = 3'b001, fill = 3'b011, heat_w = 3'b010,
    wash = 3'b110, drain = 3'b100;
```



*Grey-Code Encoding*

Note: Also requires setting STATE MACHINE ENCODING assignment to User-Encoded

# UNDEFINED STATES

**Noise and spurious events in hardware can cause state machines to enter undefined states**

**If state machines do not consider undefined states, it can cause mysterious “lock-ups” in hardware**

**Good engineering practice is to consider these states**

**Synthesis tools may require explicit coding to account for undefined states**


# 'SAFE' STATE MACHINE ??

//State transitions

```
always @(posedge clk)
    state <= next_state;
```

//Next State logic

```
always @(state or reset or door_closed or full or
    heat_demand or done or empty)
begin
    next_state = state; //default condition
    case (state)
        idle: if (door_closed) next_state = fill;
        fill: if (full) next_state = heat_w;
        heat_w: if (heat_demand==0) next_state= wash;
        wash: begin
            if (heat_demand) next_state=heat_w;
            if (done) next_state=drain;
        end
        drain: if (empty) next_state=idle;
        default: next_state = idle;
    endcase
end
```

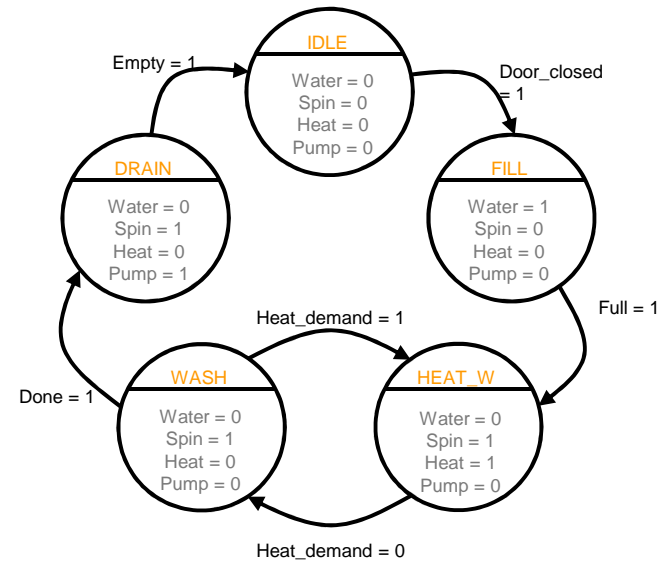


– Using default clause to cover all undeclared states

# REGISTERED OUTPUTS

**Remove glitches by adding output registers**


- Adds a stage of latency

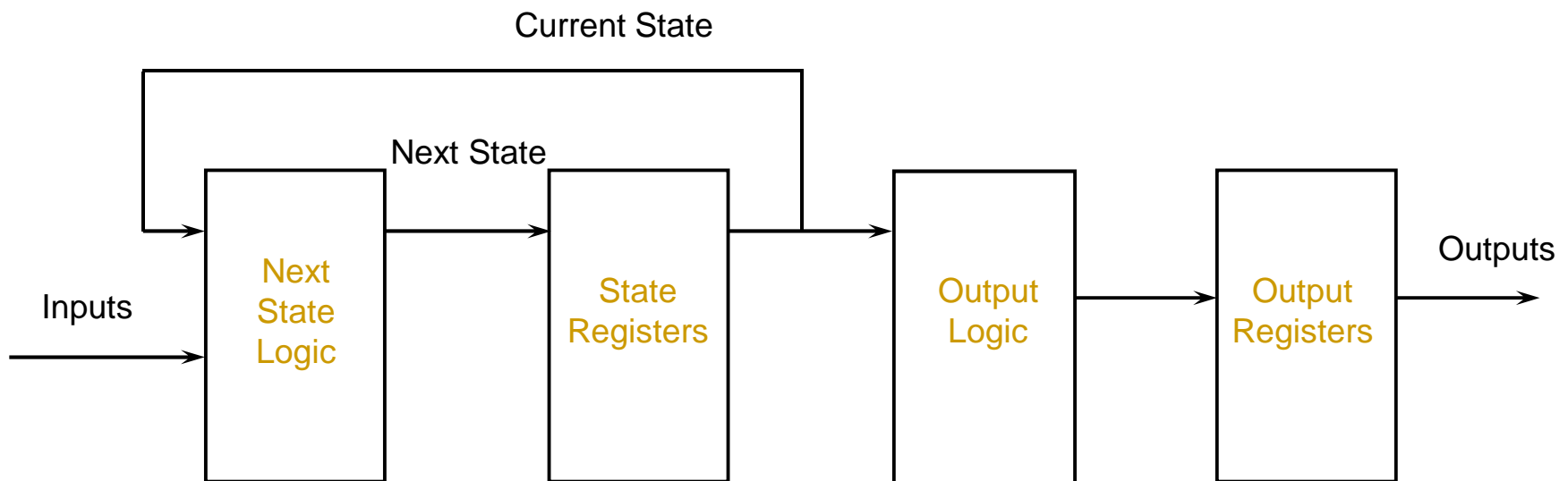

# REGISTERED OUTPUTS W/O LATENCY

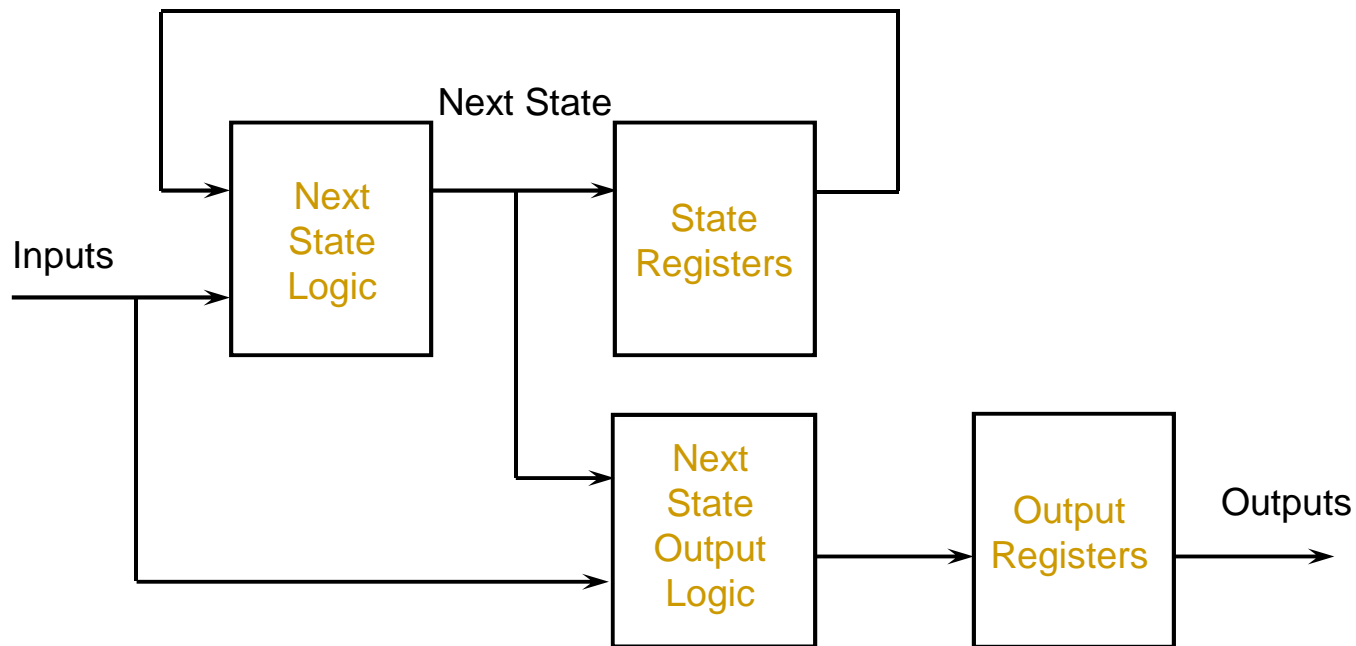
**With a Mealy machine next state outputs are a function of current state and inputs**

- This is possible because outputs are fixed between state transitions


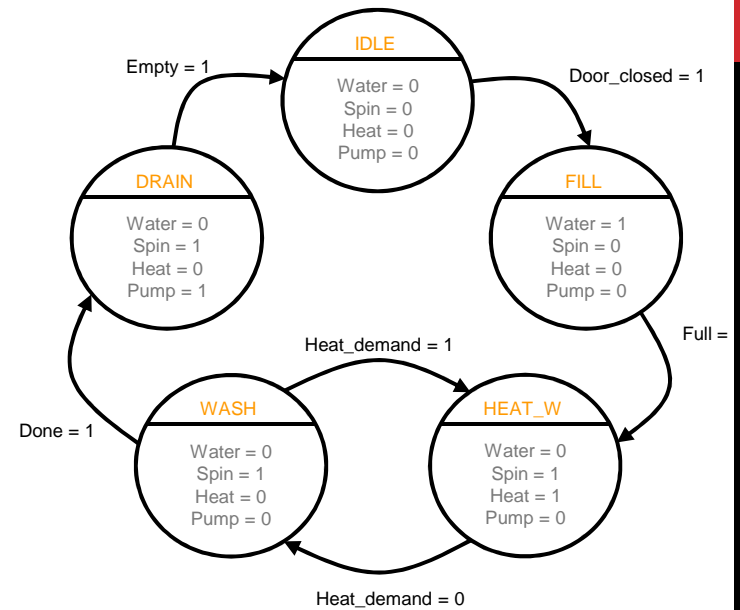
# REGISTERED OUTPUTS

```
//output logic
always @(posedge clk)
begin
    water = 0;
    spin = 0;
    heat = 0;
    pump = 0;
    case (next_state)
        idle: ;
        fill: water <= 1;
        heat_w: begin spin <= 1; heat <= 1; end
        wash: spin <= 1;
        drain: begin spin <= 1; pump <= 1; end
    endcase
end
```



# USING CUSTOM ENCODING STYLES

**Remove glitches without output registers**

**Eliminate combinatorial output logic**

**Outputs mimic state bits**

- Use additional state bits for states that do have exclusive outputs


State	Outputs	Custom Encoding
	Water Spin Heat Pump	
Idle	0 0 0 0	0000
Fill	1 0 0 0	1000
Heat_w	0 1 1 0	0110
Wash	0 1 0 0	0100
Drain	0 1 0 1	0101


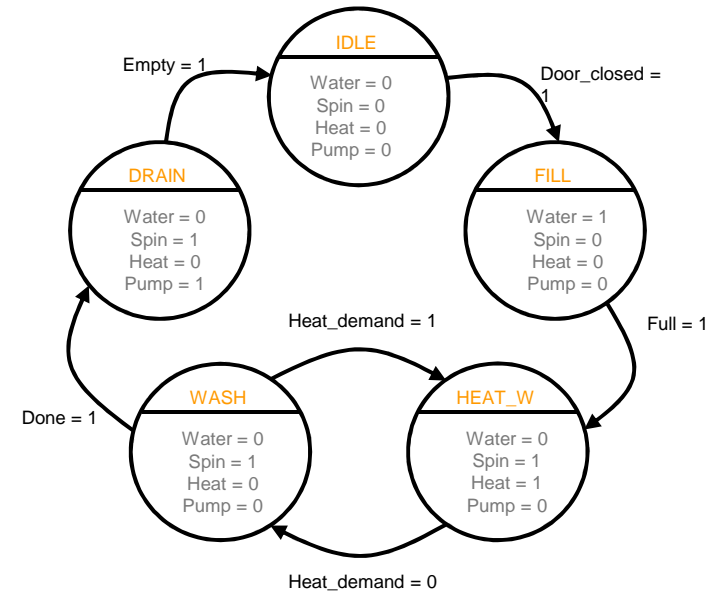
# CUSTOM STATE ENCODING

```
reg [3:0] state, next_state;  
parameter idle = 'b0000, fill = 'b1000,  
    heat_w = 'b0110, wash = 'b0100,  
    drain = 'b0101;
```

```
//output logic  
always @(state)  
begin  
    water <= state[3];  
    spin <= state[2];  
    heat <= state[1];  
    pump <= state[0];  
end
```



*Custom Encoding*


*Assign outputs to state bits*

Note: Also requires setting STATE MACHINE ENCODING assignment to User-Encoded

# EFFICIENT STATE MACHINES

 **Remove Counting, timing functions from the state machine and implement externally**



- This reduces overall logic and improves performance



# EXTERNAL COUNTER
 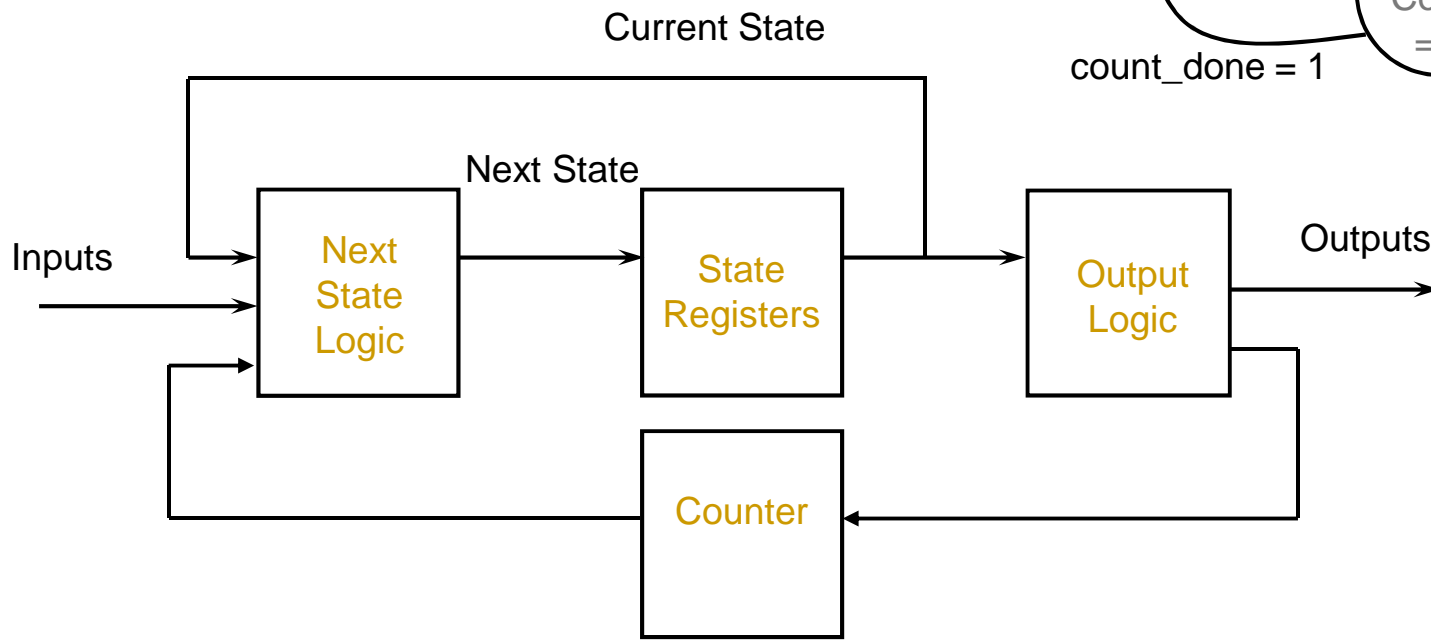
## Add outputs to control counter

- Counter overflow becomes input to state machine



# GENERAL DESIGN CONSIDERATIONS

**Write code target device in mind**

**Use synchronous design methods**

**Avoid combinatorial loops**

**Avoid gated clocks**

# LOGIC OPTIMIZATION FOR FPGA

**Balancing Operators**

**Resource Sharing**

**Logic Duplication**

**Pipelining**

# OPERATORS

**Synthesis tools replace operators with pre-defined (pre-optimized) blocks of logic**



**Designer should control when & how many operators**

# GENERATING LOGIC FROM OPERATORS


- Synthesis tools break down code into logic blocks
- They then assemble, optimize & map to hardware

```
if (sel < 10)  
    y = a + b;  
else  
    y = a + 10;
```


1 Comparator

  

2 Adders

 

1 Multiplexer

 


# BALANCING OPERATORS

## Use parenthesis to define logic groupings

- Increases performance & utilization
- Balances delay from all inputs to output
- Circuit functionality unchanged


### Unbalanced

$out = a * b * c * d;$

 

### Balanced

$out = (a * b) * (c * d);$

 




# BALANCING OPERATORS: EXAMPLE

a, b, c, d: 4-bit vectors


## Unbalanced

$$\text{out} = a * b * c * d$$

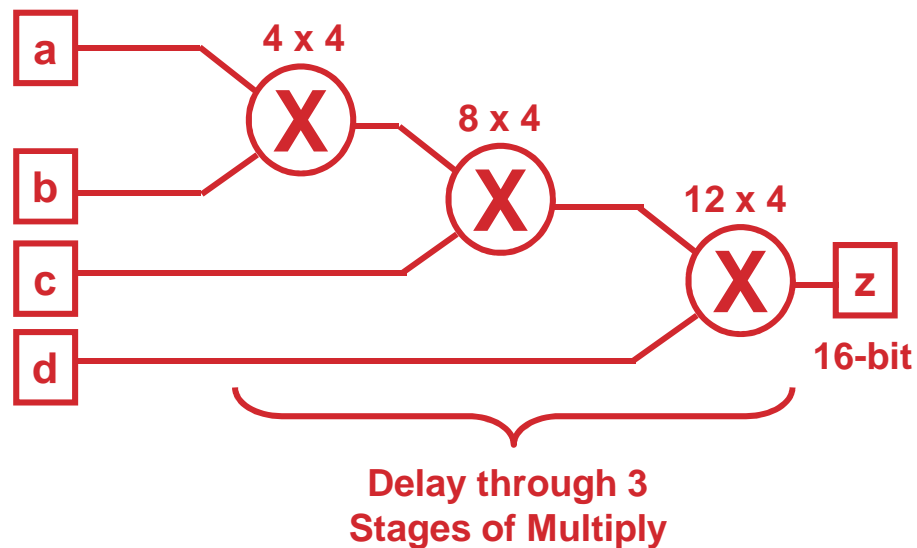

## Balanced

$$\text{out} = (a * b) * (c * d)$$

 

# RESOURCE SHARING

## **Reduces number of operators needed**

- Reduces area

## **Two types**

- Sharing operators among mutually exclusive functions
- Sharing common sub-expressions


## **Synthesis tools can perform automatic resource sharing**

- Feature can be enabled or disabled
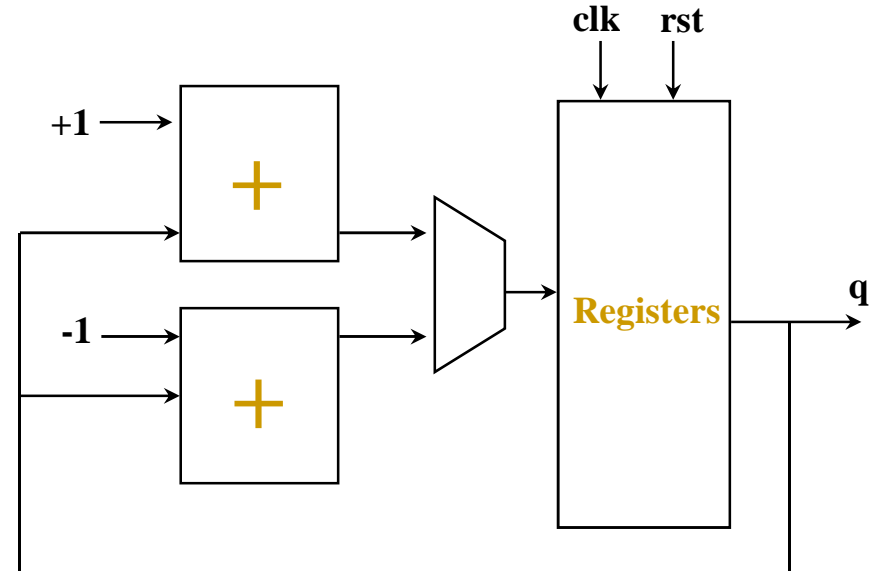
# MUTUALLY EXCLUSIVE OPERATORS

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
  
always@(posedge clk or negedge rst) begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        q <= q + 1;  
    else  
        q <= q - 1;  
    end  
endmodule
```


- Up/down counter
- EDA tool recognizes this code as a counter and will implement it efficiently, but in general it is not true!


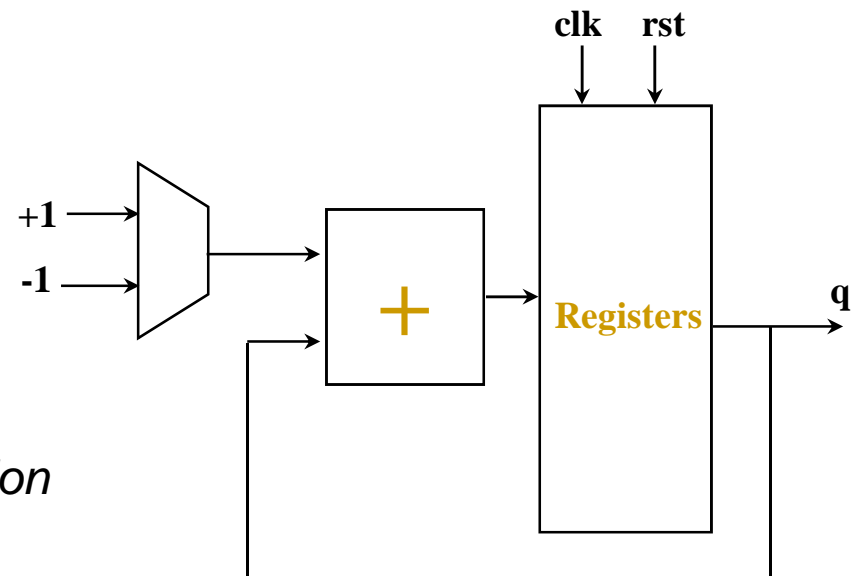
# SHARING MUTUALLY EXCLUSIVE OPERATORS

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
  
always@(posedge clk or negedge rst)  
begin  
    if (!rst)  
        q <= 0;  
    else  
        q <= q + ( updn ? 1 : -1);  
    end  
endmodule
```

- Up/down counter
- Only one adder required



*Single add operation*

# LOGIC DUPLICATION

**Intentional duplication of logic to reduce fan-out**


**Synthesis tools can perform automatically**

- User sets maximum fan-out of a node

# FAN-OUT PROBLEMS

**High fan-out puts extra loading on to signals slowing performance**


- In this case fan-out is 1 and 15

 

# CONTROLLING FAN-OUT

 **By replicating logic fan-out can be reduced**


- Worst case path now contains fan-out 3 and 5


 
# REPLICATING REGISTERS

The register at point B is replicated to reduce fan-out from this point

- Path A-B becomes slower, path B-C becomes faster
- As B-C is critical path result is improved performance






# AUTOMATIC FAN-OUT CONTROL

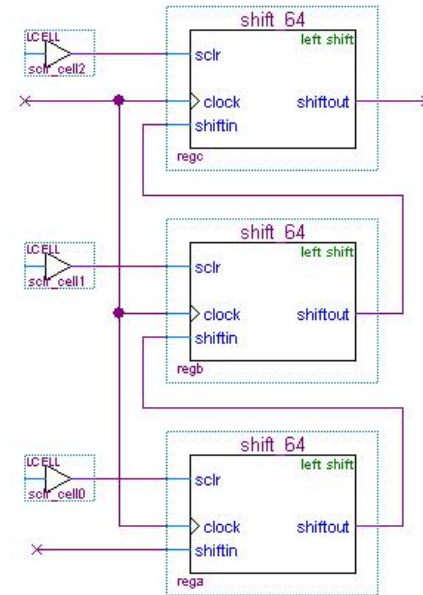**Most Synthesis tools feature options which can limit fan-out**

- Advantage: Allows easy experimentation
- Disadvantage: less control over results
  - Knowing which nodes fan-out where helps with floor-planning

```
always @(posedge clk) begin
    if (sclr2)
        regc <= 0;
    else
        regc <= {regc[62:0], regb[63]};
    if (sclr1)
        regb <= 0;
    else
        regb <= {regb[62:0], rega[63]};
    if (sclr0)
        rega <= 0;
    else
        rega <= {rega[62:0], shiftin};
end
assign shiftout = regc[63];
```



- *sclr* is replicated so that it appears 3 times
- This reduces the loading by a factor of three
- Fan-out from the previous cell has gone from 1 to 3 but this is insignificant

# PIPELINING

**Purposefully inserting register(s) into middle of combinatorial data (critical) path**

**Increases clocking speed**

**Adds levels of latency**

- More clock cycles needed to obtain output

**Some tools perform automatic pipelining**

- Same advantages/disadvantages as automatic fan-out

# ADDING SINGLE PIPELINE STAGE IN VERILOG

## Non-Pipelined

```
module test (clk, clr_n, a, b, c, d, result);
input clk, clr_n;
input [7:0] a, b, c, d;
output reg [31:0] result;
reg [7:0] atemp, btemp, ctemp, dtemp;


always @(posedge clk or negedge clr_n) begin
    if (!clr_n) begin
        atemp <= 0;
        btemp <= 0;
        ctemp <= 0;
        dtemp <= 0;
        result <= 0;
    end else begin
        atemp <= a;
        btemp <= b;
        ctemp <= c;
        dtemp <= d;
        result <= (atemp * btemp) *(ctemp *dtemp);
    end
end
endmodule
```

## Pipelined

```
module test (clk, clr_n, a, b, c, d, result);
input clk, clr_n;
input [7:0] a, b, c, d;
output reg [31:0] result;
reg [7:0] atemp, btemp, ctemp, dtemp;
reg [15:0] int1, int2;

always @(posedge clk or negedge clr_n) begin
    if (!clr_n) begin
        atemp <= 0;
        btemp <= 0;
        ctemp <= 0;
        dtemp <= 0;
        int1 <= 0;
        int2 <= 0;
        result <= 0;
    end else begin
        atemp <= a;
        btemp <= b;
        ctemp <= c;
        dtemp <= d;
        int1 <= atemp * btemp;
        int2 <= ctemp * dtemp;
        result <= int1*int2;
    end
end
endmodule
```

# PIPELINED 4-INPUT MULTIPLIER

 

# MORE SYNTHESIS GUIDELINES

**Proper use of parentheses guide the synthesis tools in eliminating common sub expressions.**

**We can duplicate the logic which generate the signal for minimizing fan-out.**

**Trade –off:- loading effect of signal is reduced thereby speeding propagation at the cost of logic and interconnect complexity.**

**Use of mode “buffer” is not recommended for Synthesis.**

- Gate level VHDL Simulation models from ASIC vendors never use the mode buffer.
- There is potential for a port mode type mismatch when using mode “buffer”. This may result into problems during integration of different blocks.

# MORE SYNTHESIS GUIDELINES

**Style of HDL coding often has a direct impact on the result the synthesis tool delivers.**

- Partitioning of designs play a very crucial role in achieving good synthesis results.
- “Synthesis tools provides best results when the critical path lies in one hierarchical block as opposed to traversing multiple hierarchical blocks.”

**Avoid OVER-constraining the design**

- Design performance suffers.
  - Critical timing paths get the best placement and fastest routing options.
  - As the number of critical path increases, the ability to obtain the design performance objective decreases.
  - Run times increase.

# MORE SYNTHESIS GUIDELINES

## **Constraining designs:-**

- Constraints are means of communicating our requirements to the synthesis and backend tools.

## **Categories of constraints are**

- Timing constraints
  - Maximum frequency
  - Duty cycle
  - Input delays
  - Output delays
  - False paths

**Run a trial without constraints to get an idea of what is possible and what is not.**

**Leave some allowance for future expansions also.**



# MORE SYNTHESIS GUIDELINES

## For best result:-

- Use technology primitives(macros) from the target technology libraries whenever possible.
- Try small designs on the target technology to find its limitations and strengths.
- Partition and design correctly.
  - Eliminate glue logic at the top level.
  - Partition block size based on the logic function, central processing unit(CPU)resources and memories.
  - Separate random logic from structure logic –data path logic.
  - It is recommended that timing-sensitive modules are separated from the area sensitive modules.
    - This allows designers to apply different optimization strategies depending on the design goals.

# MORE SYNTHESIS GUIDELINES

## **Simulate your design before synthesis**

- Logic errors that are not caught are passed on during synthesis and the synthesized results will contain the same logic errors.

## **Avoid combinational loops in the processes.**

**If a port is declared to be an integer data type, the range should be specified, else the tool will infer a 32 bit port.**

## **Avoid mixed clock edges**

- If a larger number of both positive and negative edge flip flop are required then they should be placed in different modules.

# MORE SYNTHESIS GUIDELINES

## Coding for performance

- Common mistake is to ignore hardware and start as if programming. To achieve best performance, the designer must think about hardware.
- Improve performance by:-
  - Avoiding unnecessary priority structures in logic.
  - Optimizing logic for late arriving signals.
  - Structuring arithmetic for performance.
  - Avoiding area inefficient code.
  - Buffering high fan-out signals.
  - Pipelining for high performance.

# REFERENCES

Samir Palnitkar, “Verilog HDL: A Guide to Digital Design and Synthesis” Second edition, Prentice Hall, 2003.

J. Bergeron, Writing Testbenches: Functional Verification of HDL Models, 2nd ed. Springer, 2003.

J Bhaskar, “A Verilog HDL Primer”, Third Edition, Star Galaxy Publishing, 2005

Clifford E. Cummings, – “Nonblocking Assignments in Verilog Synthesis, Coding Styles That Kill!”  
Available: <http://www.ece.cmu.edu/~ece447/s13/lib/exe/fetch.php?media=synth-verilog-cummins.pdf>

Clifford E. Cummings, – “Verilog Nonblocking Assignments with Delays, Myths & Mysteries”

Available: <http://citeseerx.ist.psu.edu/viewdoc/download?doi=10.1.1.149.3862&rep=rep1&type=pdf>

Altera - Recommended HDL Coding Styles – Altera, Aug 18 2014,  
[https://www.altera.co.jp/ja\\_JP/pdfs/literature/hb/qts/qts\\_qii51007.pdf](https://www.altera.co.jp/ja_JP/pdfs/literature/hb/qts/qts_qii51007.pdf)

Altera - Quartus II Handbook Volume 1: Design and Synthesis, May 4 2015,  
[https://www.altera.com/literature/hb/qts/qts\\_qii5v1.pdf](https://www.altera.com/literature/hb/qts/qts_qii5v1.pdf)

Xilinx Synthesis and Simulation Design Guide, Sep21 2004 ,  
[www.xilinx.com/itp/xilinx10/books/docs/sim/sim.pdf](http://www.xilinx.com/itp/xilinx10/books/docs/sim/sim.pdf)

Philippe Garrault and Brian Philofsky- “HDL Coding Practices to Accelerate Design Performance”  
Jan 6 2006, [https://www.xilinx.com/support/documentation/white\\_papers/wp231.pdf](https://www.xilinx.com/support/documentation/white_papers/wp231.pdf)

“SystemVerilog – UNIFIED HARDWARE DESIGN, SPECIFICATION, AND VERIFICATION LANGUAGE” –  
The IEEE 1800-2012 LRM, Web link: <http://standards.ieee.org/getieee/1800/download/1800-2012.pdf>